

Lecture 1 - 8th Jan

Circuit Variables and Elements

Voltage

b charge (q) → electrons or ions

charges create electric fields \Rightarrow forces \Rightarrow work (energy).

$$\cdot V = \frac{dW}{dq} \quad (\text{"amount of work per charge"})$$


$$V = J/C$$

• V = Voltage [$V \rightarrow$ volts]

• W = Energy [$J \rightarrow$ joules]

• q = Charge [$C \rightarrow$ coulombs].

Current : Flow of positive charge


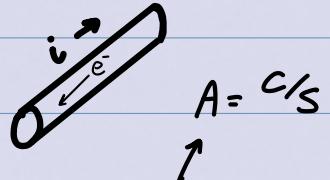


$$\cdot i = \frac{dq}{dt} \quad (\text{"charge per time"}) \Rightarrow [A \rightarrow \text{amperes}]$$

Lecture 2: 10th Jan


$$\text{Power : } \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V \cdot i = P. \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{Power : Voltage} \times \text{current}$$
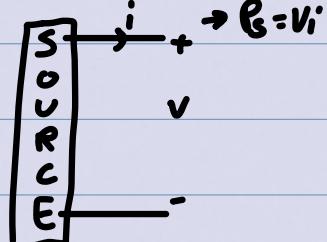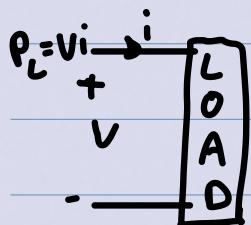
$$\hookrightarrow P = Vi \quad [W \rightarrow \text{watts}]$$







$$\rightarrow P_L = P_S.$$

Example:

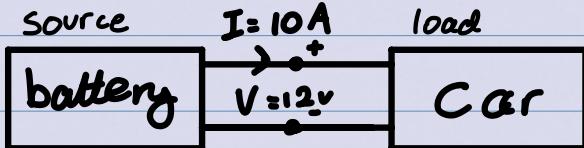

Example :

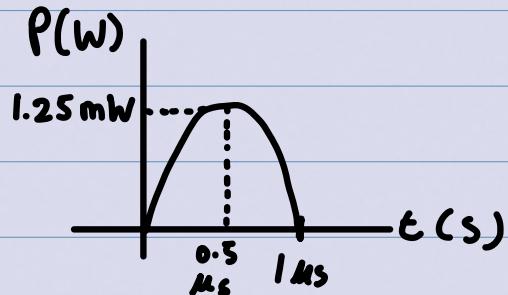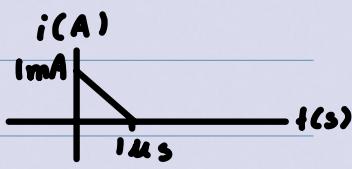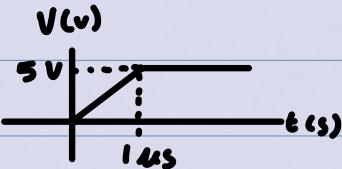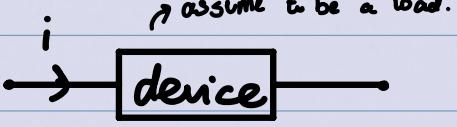

$$P_{max} = V(0.5\mu s) \times i(0.5\mu s)$$

$$\frac{5}{2}V \cdot \frac{1}{2}mA = 1.25mW$$

Ideal Sources:

• Independent Source:



Voltage and current sources.

In a voltage source, voltage is defined but current is unknown. The opposite is true for a current source.

Dependent source:



.

.

.

$$R = \frac{V}{i} \quad \left[\frac{V}{A} = \Omega \right] \quad (\text{resistance})$$

these elements always absorb power, not produce it!

$$G = \frac{1}{R} = \frac{i}{V} \quad \left[\frac{A}{V} = \Omega^{-1} \right] \quad (\text{conductance})$$

$$\therefore P = Vi = R i^2 = \frac{V^2}{R} = GV^2$$


Kirchoff's Laws:

Node \rightarrow connecting point w/ 3 or more wires

Loop \rightarrow window panes

Branches \rightarrow elements
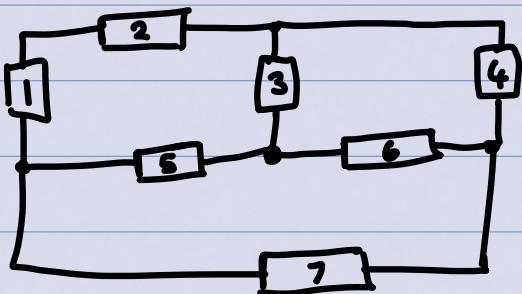
$$KCL: \sum_{\text{nodes}} i_{\text{branches}} = 0.$$



$$KVL: \sum_{\text{loop}} V_{\text{branches}} = 0.$$


- For N resistors in series, $R_{\text{eq}} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$

Also, $V_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} V$ the voltage drop across the n^{th} resistor!


- For N resistors in parallel, $R_{\text{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)^{-1}$

If $R_1 = R_2 = \dots = R_n$, then $R_{\text{eq}} = \frac{R}{n}$

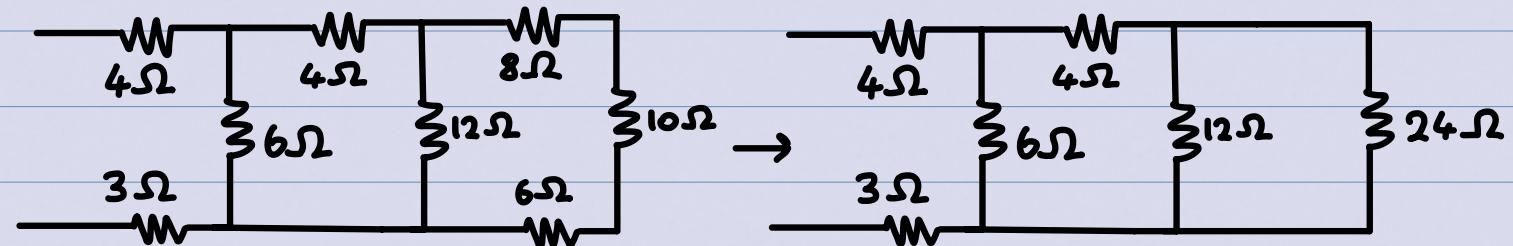Example: find R_{eq} for the following circuit:




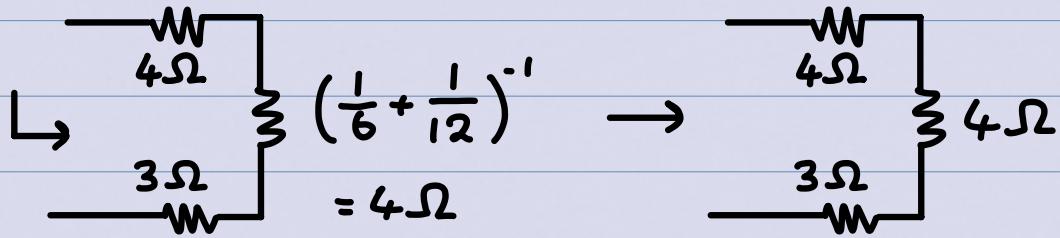\hookrightarrow $\frac{1}{R_{\text{eq}}} = \frac{1}{12} + \frac{1}{24} = \frac{1}{8}$ $\Rightarrow R_{\text{eq}} = 8\Omega$



$$\therefore R_{\text{eq}} = 4 + 4 + 3 = 11 \Omega$$

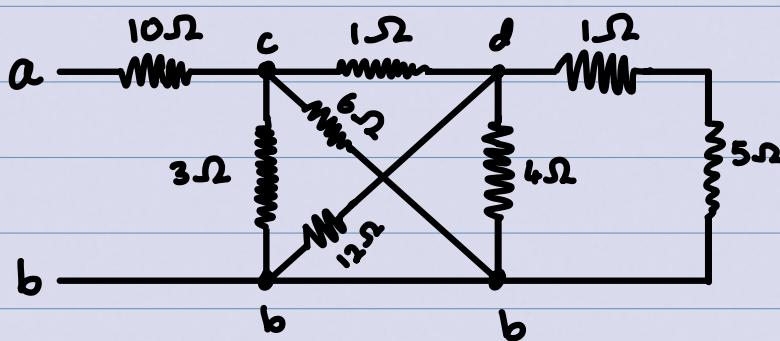Example: Find R_{ab} in the following circuit:



both nodes b at the bottom are the same, as there is no voltage drop between them!


the 3Ω and 6Ω resistors are in parallel, since they are both connected to nodes b and c!

$$\therefore R_{3,6} = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = \left(\frac{3}{6} \right)^{-1} = 2 \Omega .$$

Similarly, the 4Ω and 12Ω resistors are also in parallel, as they are both connected to nodes b and d.

$$\therefore R_{4,12} = \left(\frac{1}{4} + \frac{1}{12} \right)^{-1} = \left(\frac{4}{12} \right)^{-1} = 3 \Omega .$$

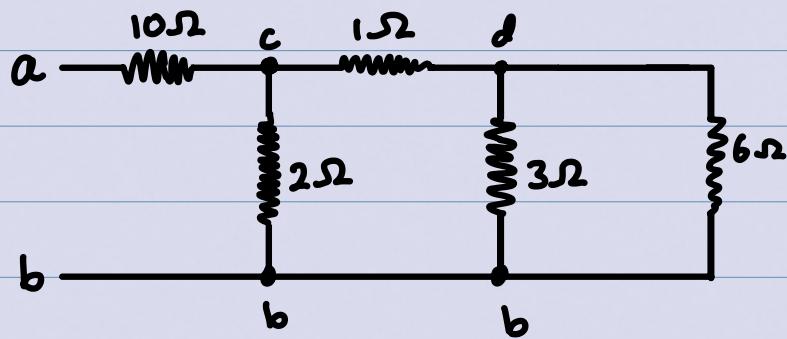
So, the circuit can be re-drawn as follows:




From here, it's a simple circuit:

$$R_{ab} = 10 + \left(\frac{1}{2} + \frac{1}{1 + (\frac{1}{3} + \frac{1}{6})^{-1}} \right)^{-1} = 11.2 \Omega$$

Wye - Delta Transformations

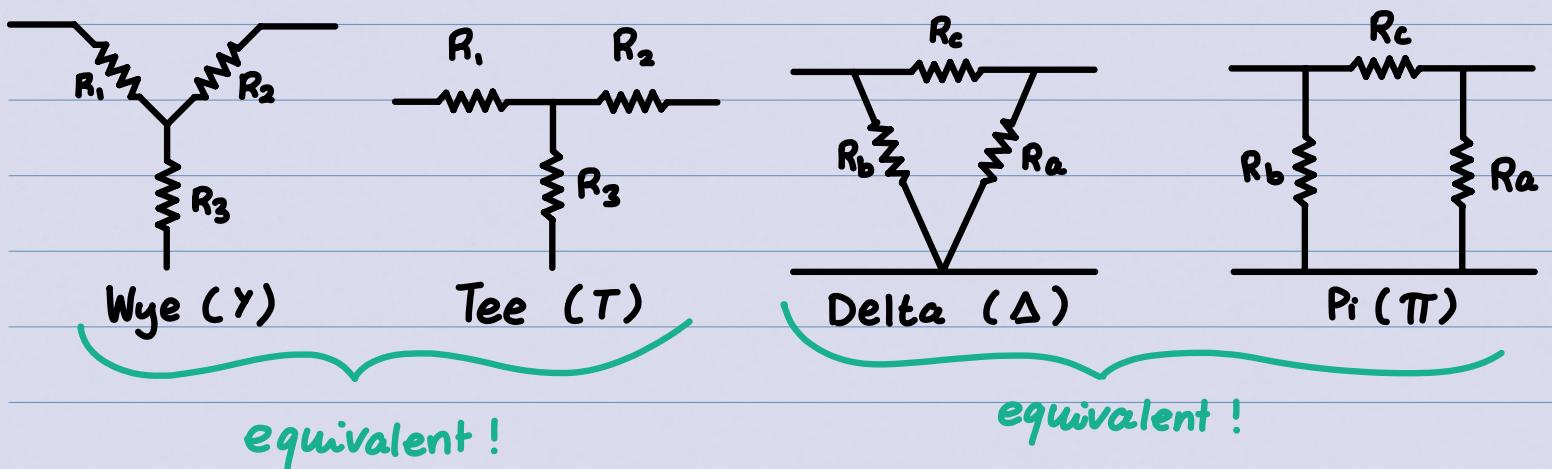

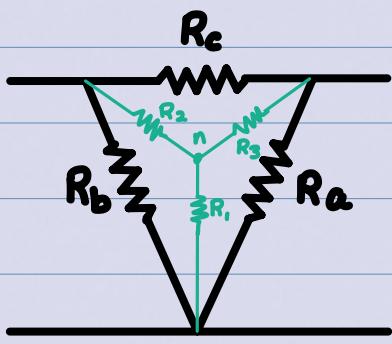Generally, we want to convert Δ networks to γ networks. To do so, we superimpose a new central node n in the center, and calculate the new resistances.



We want to calculate R_1 , R_2 , and R_3 such that the system is the same.

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}, \quad R_2 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

- Each resistor in the γ network is the product of the resistors in the two adjacent Δ branches, divided by

the sum of the three Δ resistors.

However, sometimes it might be helpful to transform the other way ($\gamma \rightarrow \Delta$).

$$\downarrow R_a = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_1}, \quad R_b = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_2}, \quad R_c = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_3}$$

- Each resistor in the Δ network is the sum of all possible products of two γ resistors, divided by the opposite γ resistor.


Nodal Analysis without Voltage Sources:

- If the circuit has no voltage sources,
 - Select a node as the reference node. Assign voltages V_1, V_2, \dots, V_{n-1} to the remaining $n-1$ nodes.
 - Apply KCL to each of the $n-1$ nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
 - Solve the resulting simultaneous equations to obtain the unknown node voltages.
- The reference node is commonly called the ground, since it is assumed to have 0 potential.

It can be indicated by:



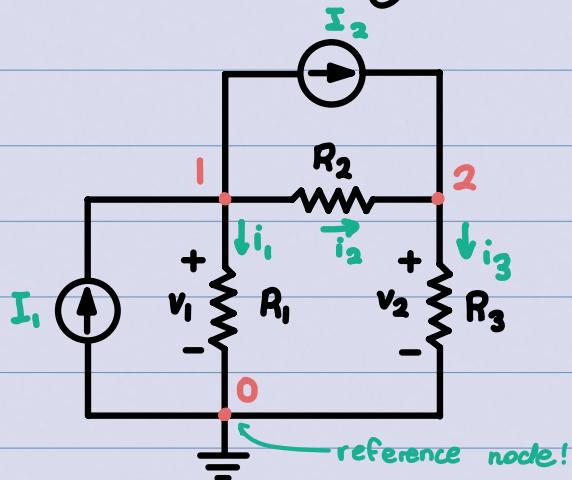Example: perform nodal analysis on the following circuit.




Performing KCL at node 1: $I_1 = I_2 + i_2 + i_1$
at node 2: $i_2 + I_2 = i_3$

$$I_1 = I_2 + i_2 + i_1 : I_1 = I_2 + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_0}{R_1} \rightarrow V_0 = 0, \text{ since it is the reference node!}$$

$$i_2 + I_2 = i_3 : \frac{V_1 - V_2}{R_2} + I_2 = \frac{V_2 - V_0}{R_3}$$

$$\hookrightarrow I_1 = I_2 + \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1}, \quad \frac{V_1 - V_2}{R_2} + I_2 = \frac{V_2}{R_3}$$

Example: calculate the node voltages:

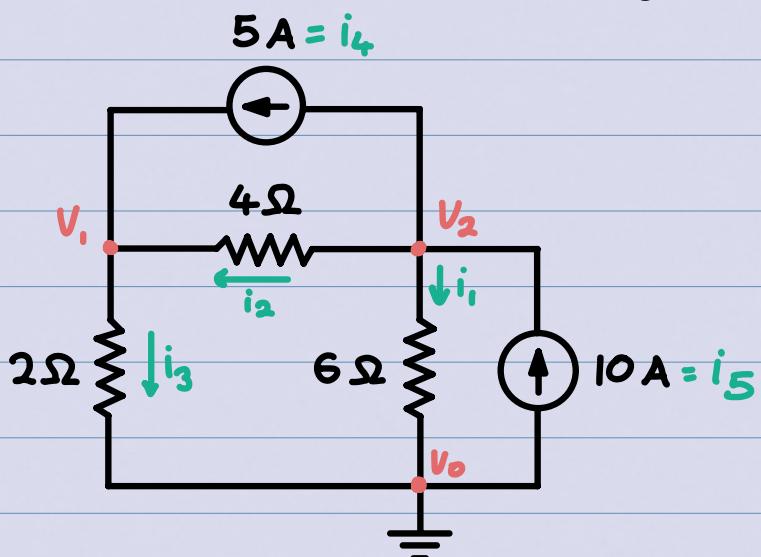

KCL at node 1: $i_4 + i_2 = i_3$

$$\text{node 2: } i_5 = i_1 + i_2 + i_4$$

$$\hookrightarrow 5 + i_2 = i_3 , \quad 10 = i_1 + i_2 + 5$$

$$5 + \frac{V_2 - V_1}{4} = \frac{V_1 - 0}{2} , \quad 5 = \frac{V_2 - 0}{6} + \frac{V_2 - V_1}{4}$$

$$5 + \frac{V_2 - V_1}{4} = \frac{V_1}{2} , \quad 5 = \frac{V_2}{6} + \frac{V_2 - V_1}{4} \rightarrow \begin{matrix} \text{from here,} \\ \text{simple system of} \\ \text{equations!} \end{matrix}$$

$$\downarrow \\ V_1 = 10 + \frac{V_2 - V_1}{2} \rightarrow 2V_1 = 20 + V_2 - V_1 \rightarrow V_1 = \frac{20 + V_2}{3}$$

$$60 = 2V_2 + 3V_2 - 3V_1 \rightarrow 60 = 5V_2 - 20 - V_2$$

$$\therefore 80 = 4V_2 \rightarrow V_2 = 20, V_1 = 40/3 !$$


- Current always flows from a higher potential to a lower potential in a resistor.
- The number of nonreference nodes is equal to the number of independent equations we derive.

Nodal Analysis with Voltage Sources:

- Case 1: if a voltage source is connected between the reference node and a nonreference node, simply set the voltage at the nonreference node equal to the voltage of the voltage source.
- Case 2: if a voltage source is connected between two nonreference nodes, these two nodes form a generalized node or a supernode \rightarrow apply KCL


and KVL to determine node voltages.

Example of possible supernode :

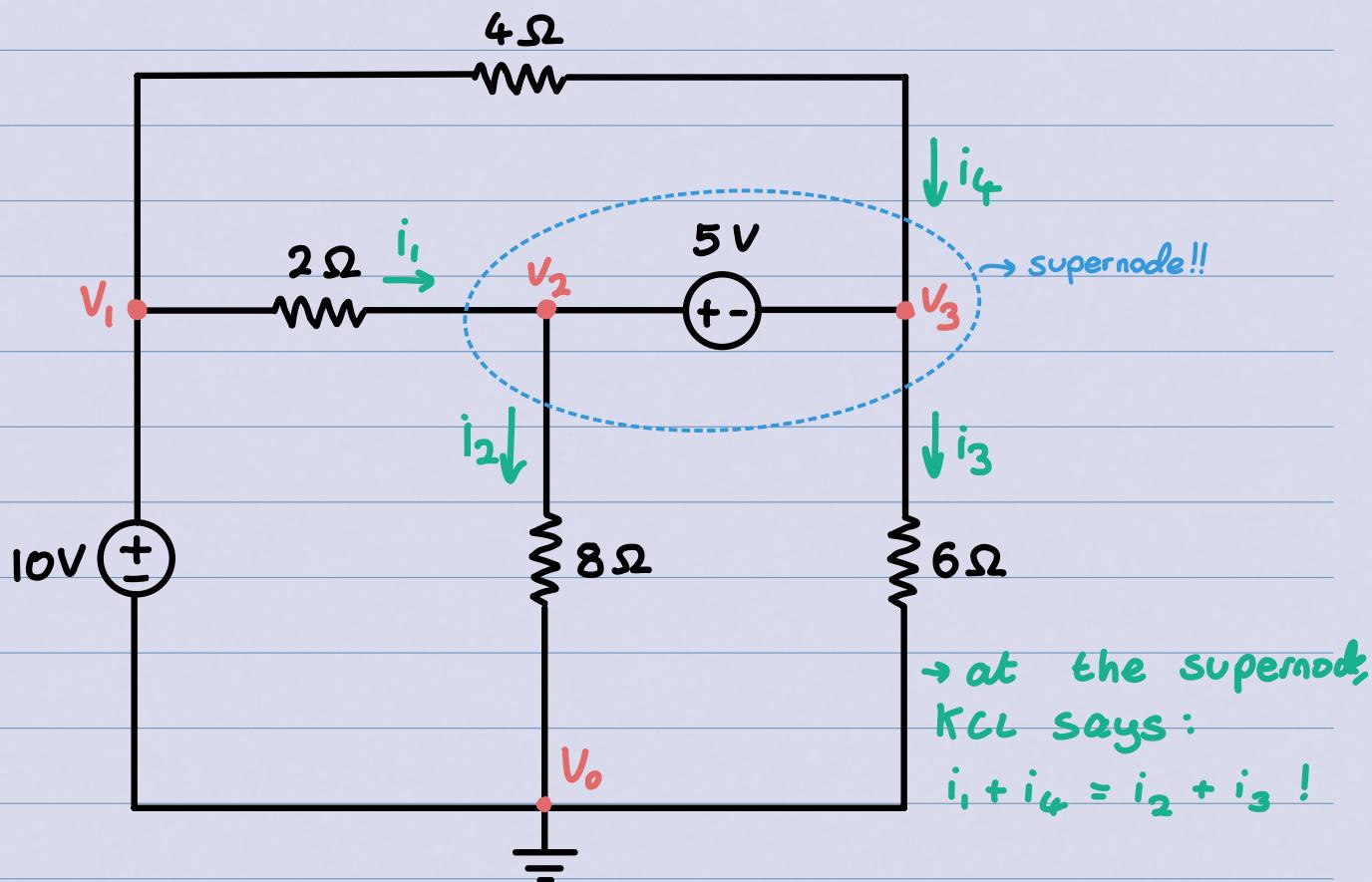

- A supernode may be regarded as a closed surface enclosing the voltage source + the two nodes.

Example: Find the node voltages :

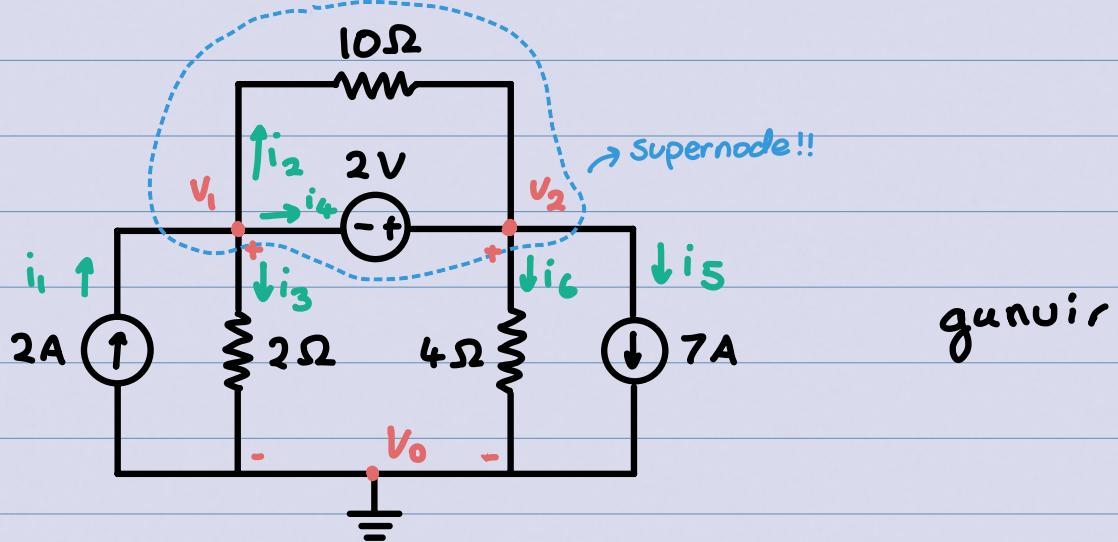

KCL on the supernode: $i_1 = i_3 + i_6 + i_5 \rightarrow 2 = i_3 + i_6 + 7$

$$\hookrightarrow 2 = \frac{V_1 - 0}{2} + \frac{V_2 - 0}{4} + 7$$

$$\hookrightarrow 8 = 2V_1 + V_2 + 28 \rightarrow 2V_1 + V_2 = -20$$

Then, using KVL on the central loop: $-2i_3 - 2 + 4i_6 = 0$

$$-2i_3 = -V_1 \text{ and } 4i_6 = V_2.$$


Simple system
of equations
from here!

$$\therefore 2V_1 + V_2 = -20, \quad V_2 = 2 + V_1$$

$$\hookrightarrow 2V_1 + V_1 + 2 = -20 \rightarrow 3V_1 = -22 \rightarrow V_1 = -\frac{22}{3} V.$$


$$\therefore V_1 = -\frac{22}{3} V \text{ and } V_2 = -\frac{16}{3} V.$$

Example: Find the node voltages

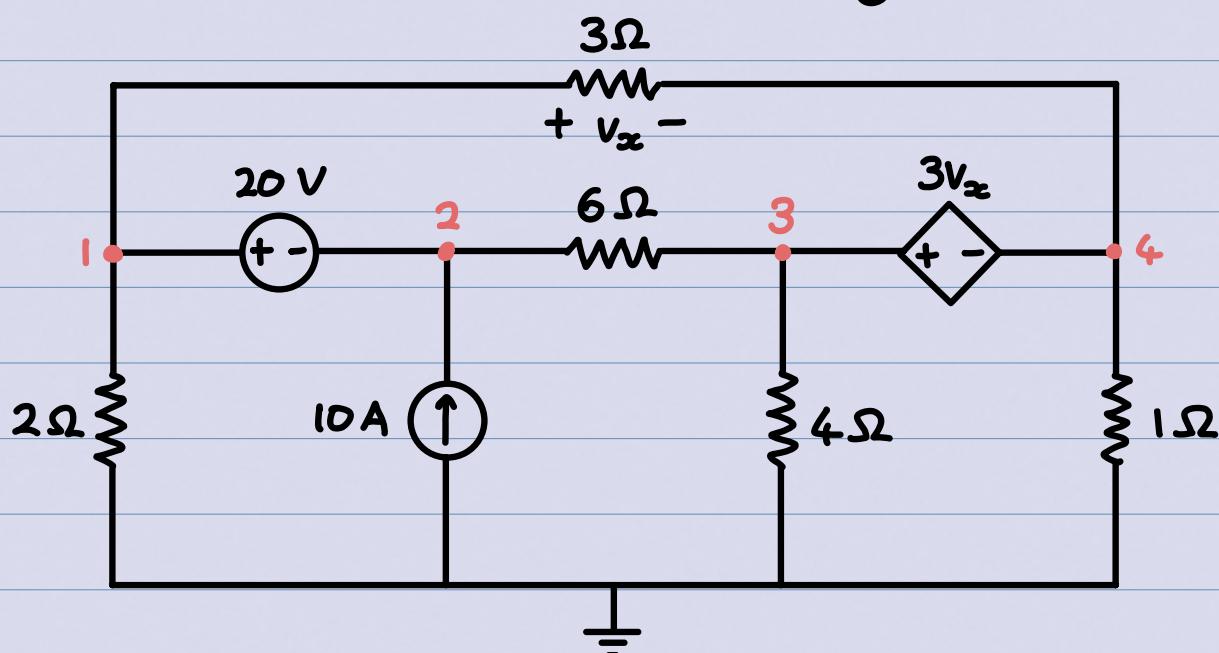

Nodes 1/2 and nodes 3/4 are supernodes!



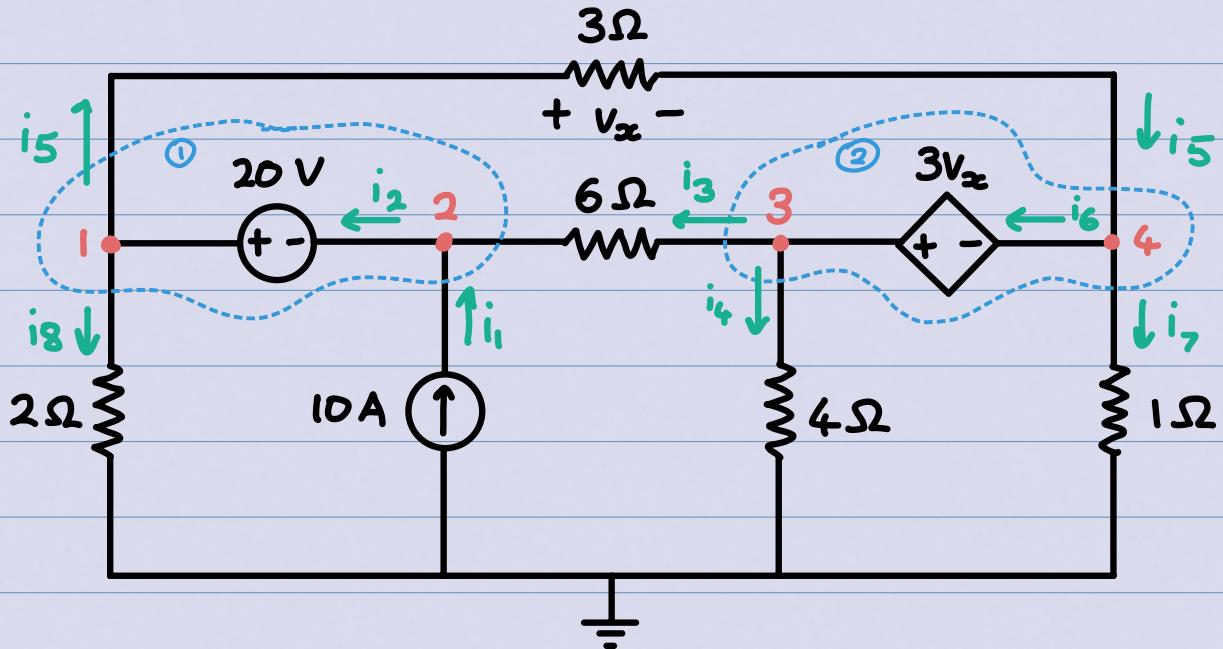

KCL in supernode 1: $i_1 + i_3 = i_6 + i_8 \rightarrow i_3 + 10 = i_5 + i_8$

KCL in supernode 2: $i_5 = i_3 + i_4 + i_7$

$$i_3 + 10 = i_5 + i_8 \rightarrow \frac{V_3 - V_2}{6} + 10 = \frac{V_1 - V_4}{3} + \frac{V_1 - 0}{2}$$

$$\hookrightarrow V_3 - V_2 + 60 = 2V_1 - V_4 + 3V_1$$

$$\hookrightarrow 5V_1 + V_2 - V_3 - V_4 = 60$$

$$i_5 = i_3 + i_4 + i_7 \rightarrow \frac{V_1 - V_4}{3} = \frac{V_3 - V_2}{6} + \frac{V_3 - 0}{4} + \frac{V_4 - 0}{1}$$

$$\hookrightarrow 4V_1 - 4V_4 = 2V_3 - 2V_2 + 3V_3 + 12V_4$$


$$\hookrightarrow 4V_1 + 2V_2 - 5V_3 - 16V_4 = 0$$

Now, using KVL as shown:

$$① -V_1 + 20 + V_2 = 0$$

$$② -V_3 + 3V_x + V_4 = 0$$

$$③ V_x - 3V_x + 6i_3 - 20 = 0$$

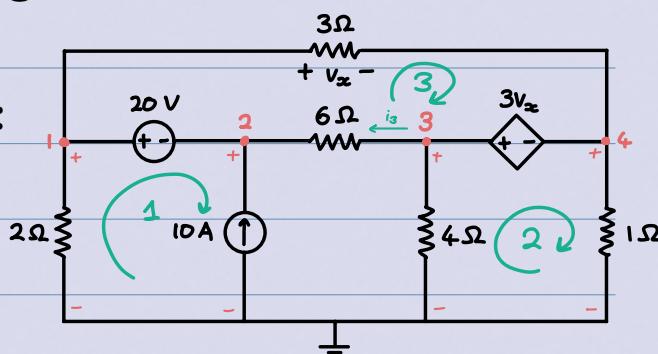

but, $V_1 - V_x = V_4$, so:

$$V_x = V_1 - V_4 !$$

∴ we have:

$$5V_1 + V_2 - V_3 - V_4 = 60$$

$$4V_1 + 2V_2 - 5V_3 - 16V_4 = 0$$

$$V_1 = V_2 + 20$$

$$V_3 = 3V_1 - 2V_4$$

$$-2V_1 - 6V_2 + 6V_3 + 2V_4 = 0$$

also, $6i_3 = V_3 - V_4$!


5 equations,
4 unknowns!

$$\therefore V_1 = \frac{240}{9} V, V_2 = \frac{20}{3} V, V_3 = \frac{520}{3} V, V_4 = -\frac{140}{3} V!$$

Planar Circuit: can be drawn in a plane with no branches crossing one another.

↳ a circuit may have crossing branches and still be planar if it can be redrawn to avoid crossing branches.

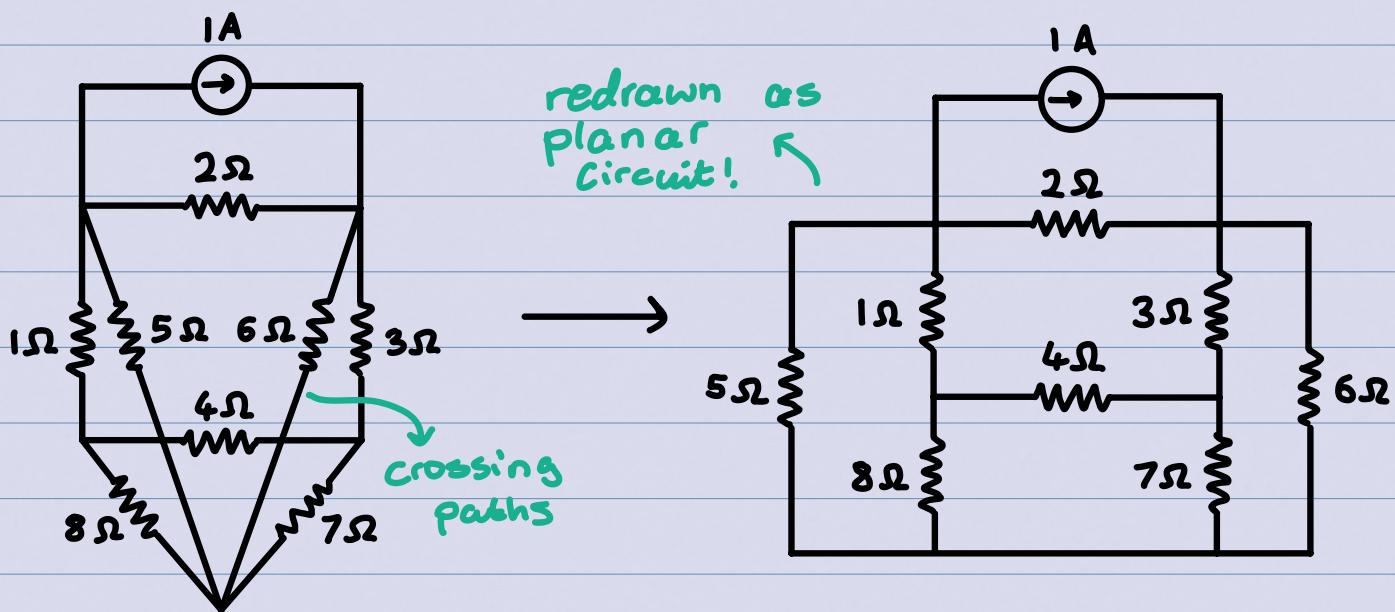Example: show that this circuit is planar:



• **Mesh:** a loop that does not contain any other loops within it.


Mesh Analysis: applies KVL to find currents.

↳ only applies to circuits that are planar!

↓

- 1) Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
- 2) Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
- 3) Solve the resulting n simultaneous equations.

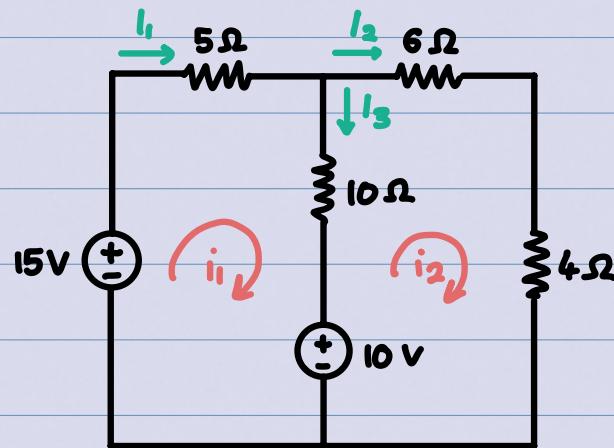Example: Find the branch currents using mesh analysis.



$$i_1 = i_2 + i_3$$
$$\hookrightarrow i_3 = i_1 - i_2$$

KVL on mesh 1: $-15 + 5i_1 + 10i_3 + 10 = 0$
 $-15 + 5i_1 + 10i_1 - 10i_2 + 10 = 0$
 $-5 + 15i_1 - 10i_2 = 0$
 $\hookrightarrow 3i_1 - 2i_2 = 1.$

KVL on mesh 2: $-10 - 10i_3 + 6i_2 + 4i_2 = 0$
 $-10 - 10i_1 + 10i_2 + 10i_2 = 0$
 $20i_2 - 10i_1 = 10$
 $\hookrightarrow i_1 = 2i_2 - 1.$


Simple system
of equations!

$$\therefore I_1 = i_1 = 1A, I_2 = i_2 = 1A, I_3 = i_1 - i_2 = 0A !$$

Mesh Analysis with current sources

- Case 1: when a current source exists only in one mesh. Set the current of that mesh to the current source, and write mesh equations for the remaining meshes.
- Case 2: when a current source exists between two or more meshes, we create a supermesh by excluding the current source and any elements connected in series with it.

Example: mesh analysis case 1 circuit.

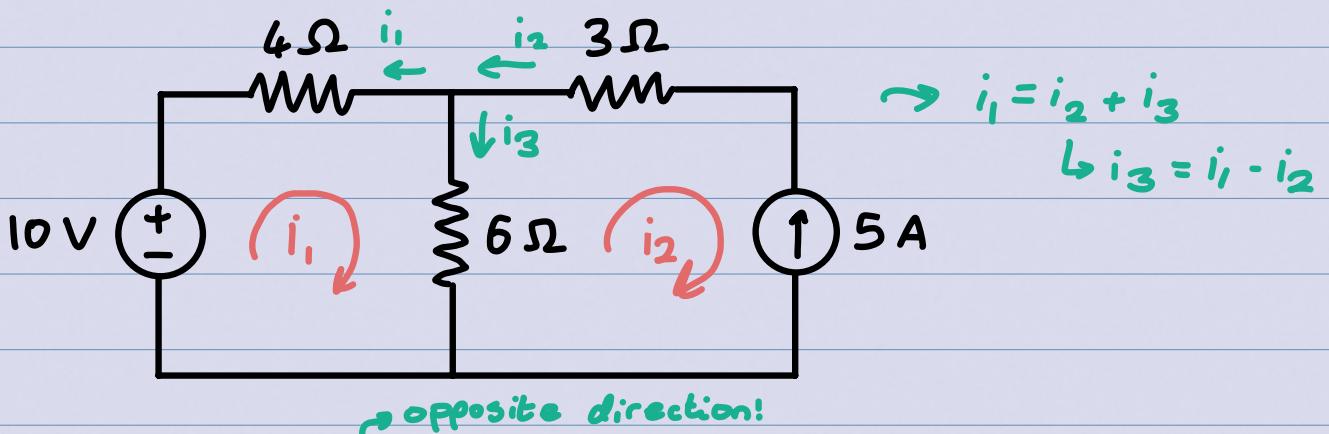


↳ i_2 is set to $-5A$, and we perform KVL on mesh 1 as follows: $-10 + 4i_1 + 6i_3 = 0$

$$\hookrightarrow -10 + 4i_1 + 6i_1 - 6i_2 = 0 \rightarrow 20 = -10i_1 \rightarrow i_1 = -2$$

$$\therefore i_1 = -2A, i_2 = -5A, i_3 = 3A$$

- Note: be very careful setting the mesh current! negative if it's flowing the other way!

Example: mesh analysis case 2 circuit

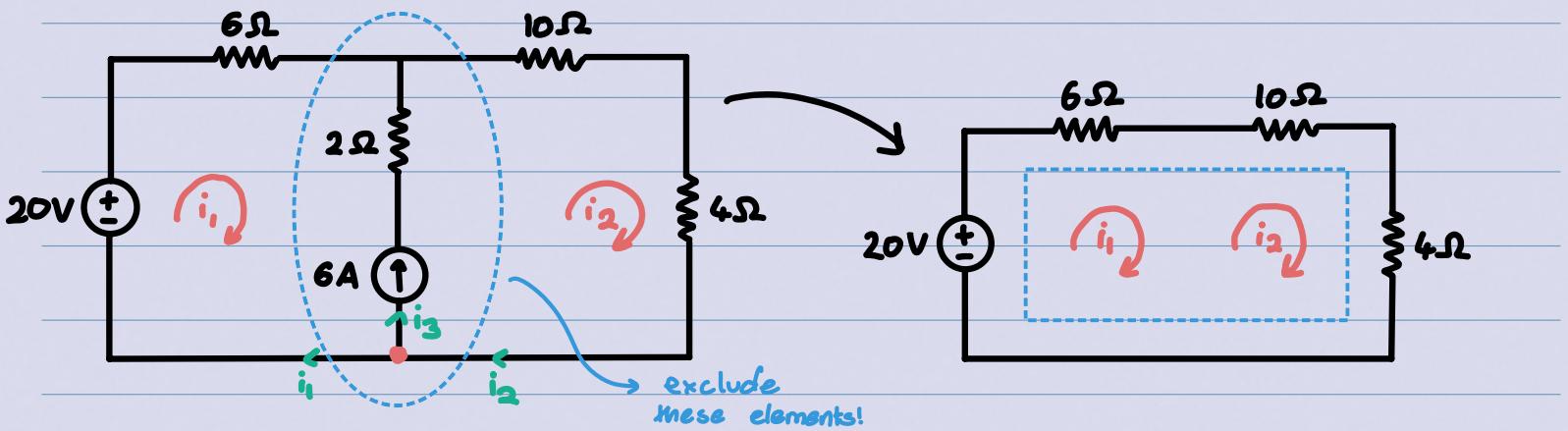

performing KVL on the supermesh: $-20 + 6i_1 + 10i_2 + 4i_2 = 0$

$$\hookrightarrow 6i_1 + 14i_2 = 20 \rightarrow 3i_1 + 7i_2 = 10.$$

Now, apply KCL to a node in the branch where the two meshes intersect: $i_2 = i_1 + 6$

$$\therefore i_1 = -3.2\text{ A}, \text{ and } i_2 = 2.8\text{ A}.$$

• Notes:


- ↳ the current source in the supermesh provides the constraint equation necessary to solve for the mesh currents

- ↳ supermesh has no current of its own.

- ↳ A supermesh requires the application of both KCL and KVL.

- Linear Circuit: output is linearly related (or directly proportional) to its input.

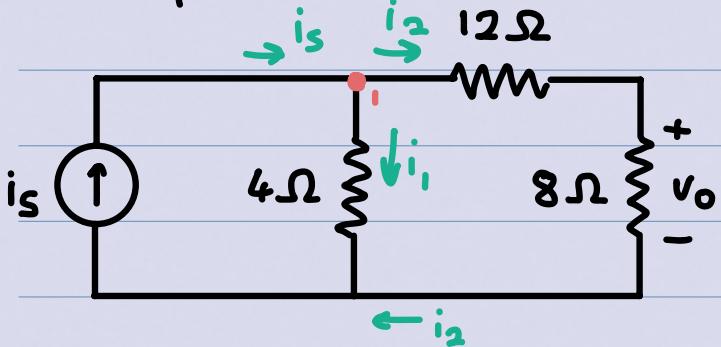Example: Find V_o when $i_s = 30 \text{ A}$ and $i_s = 45 \text{ A}$.



$$\text{KVL: } 12i_2 + 8i_2 - 4i_1 = 0$$

$$\hookrightarrow 5i_2 = i_1$$

$$\text{KCL: } i_s = i_1 + i_2$$

$$\therefore 6i_2 = i_s \rightarrow i_2 = \frac{i_s}{6}.$$

$$\text{we know that } V_o = 8i_2, \text{ so } V_o = \frac{4i_s}{3}.$$

$$\text{when } i_s = 30: V_o = \frac{4(30)}{3} \rightarrow V_o = 40V.$$

$$\text{when } i_s = 45: V_o = \frac{4(45)}{3} \rightarrow V_o = 60V$$

Since the difference in these voltages is proportional to the difference in the inputs (i_s), this circuit is linear!


Superposition: the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or current through) that element due to each independent source acting alone.

Steps to Apply Superposition:

- 1) Turn off all independent sources except one (turn off means set to 0V or 0A). Find the output due to the active source.
- 2) Repeat step 1 for all the independent sources.
- 3) Find the total contribution by summing all the contributions due to the independent sources.

• Note: Superposition only works on linear Circuits!


Example: Use superposition to find V :

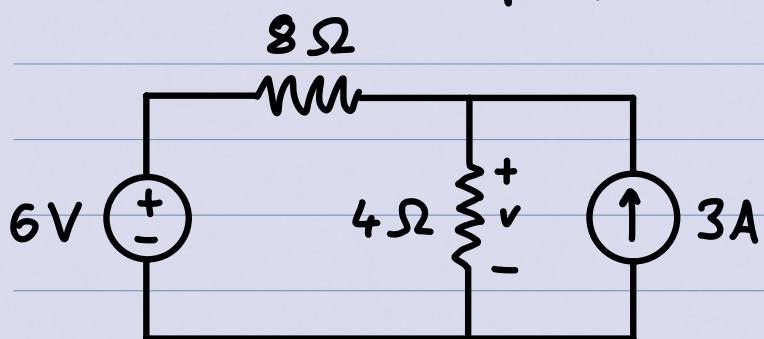


let $V = V_1 + V_2$, where

V_1 is the contribution from the 6V voltage source, and V_2 is the contribution from the 3A current source.

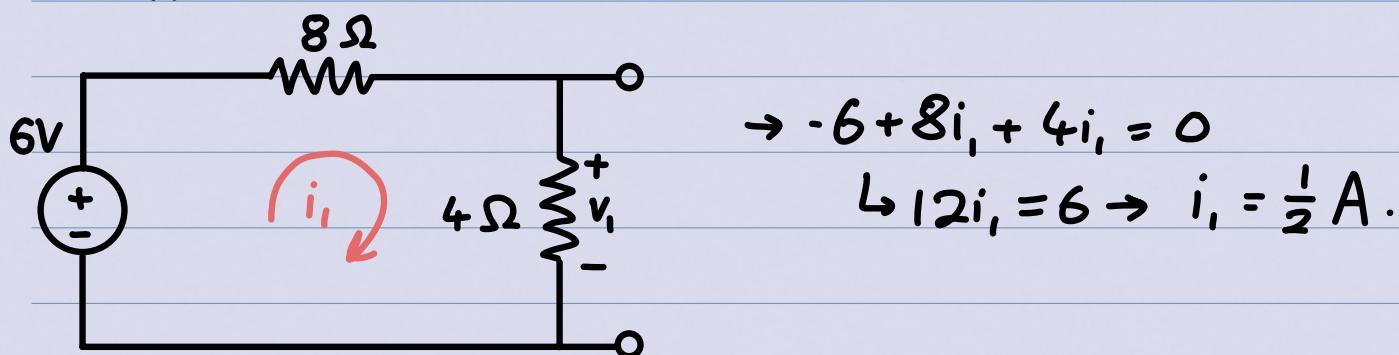to obtain V_1 , we set the current source to 0A and do KVL:



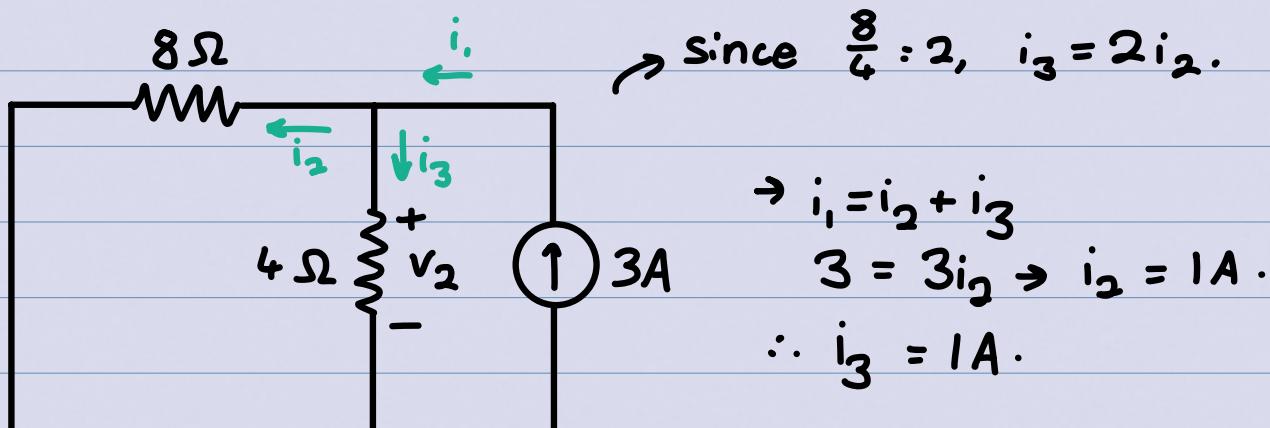
to obtain V_2 , we set the voltage source to 1A and do KCL:



$$V_1 : 4\Omega \cdot \frac{1}{2} \text{ A} = 2 \text{ V}, \quad V_2 = 4\Omega \cdot 2 \text{ A} = 8 \text{ V.}$$

$$\therefore V = V_1 + V_2 = 2 + 8 = 10 \text{ V.}$$

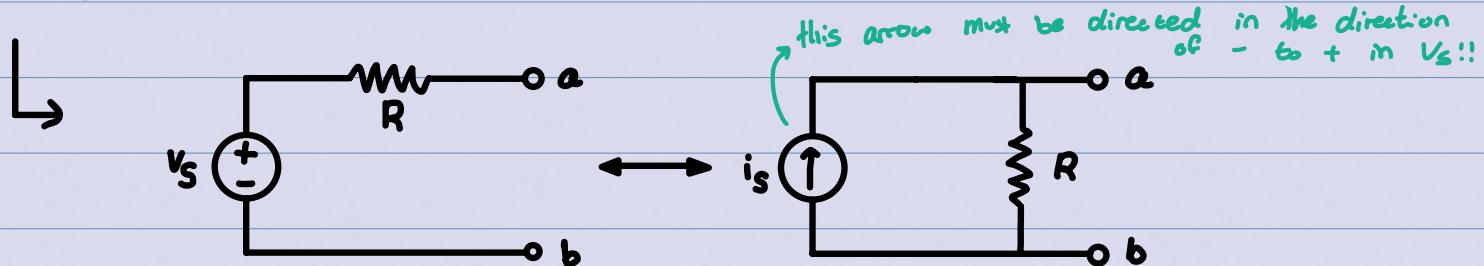
Source Transformation: the process of replacing a voltage source V_s in series with a resistor R by a current source in parallel with a resistor R , or vice versa.




Source Transformations require: $V_s = i_s R$ or $i_s = \frac{V_s}{R}$

- This technique also works for dependent sources!

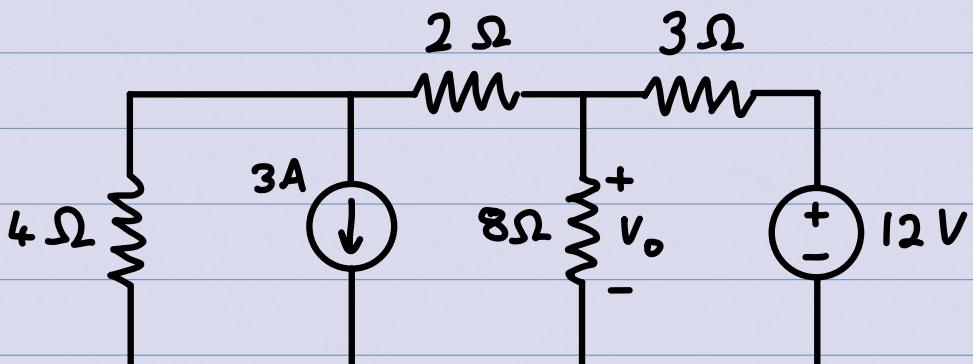
Example: Use source transformation to find V_o :




Transforming the 3A current source:

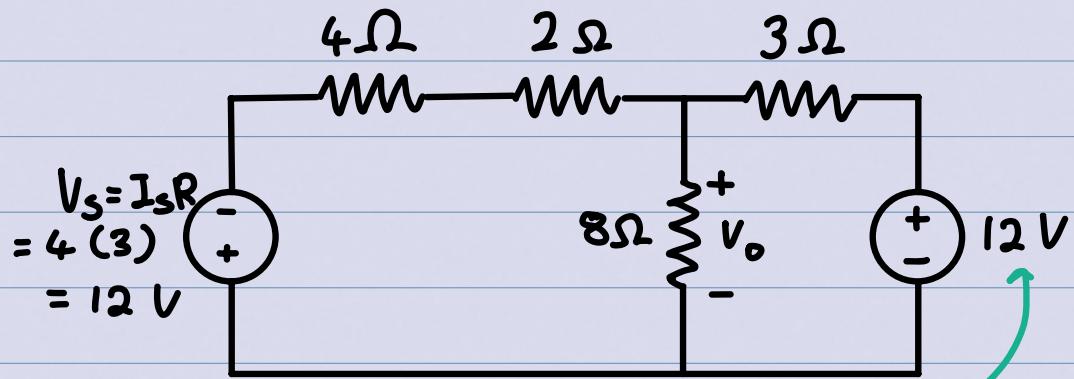

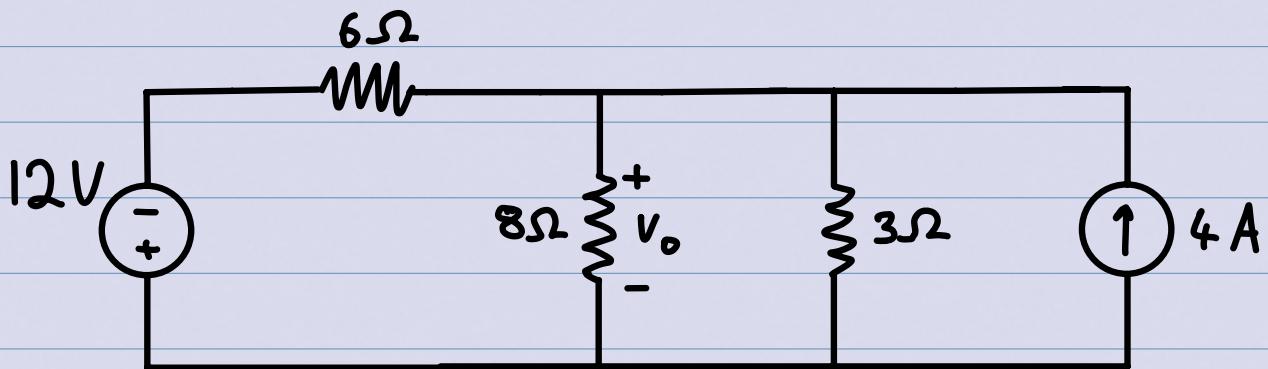Transforming the 12V (right) voltage source:




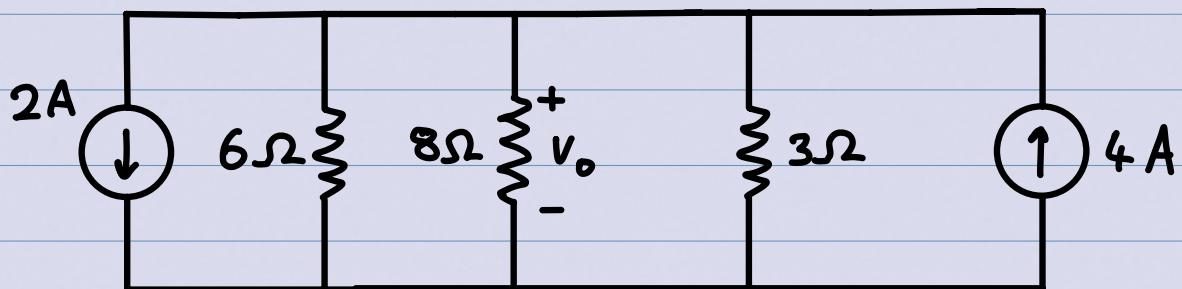Now, transforming the 12V voltage source again! :




Finding the equiv. resistance of the 3Ω and 6Ω resistors:
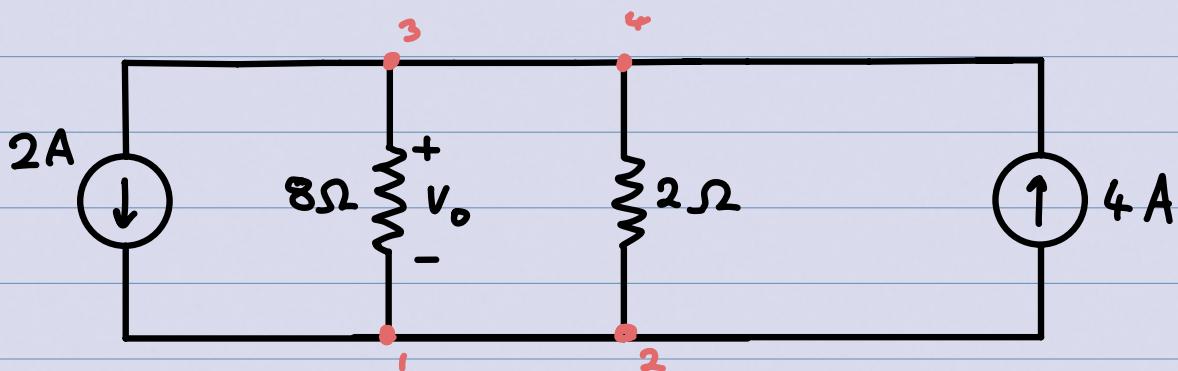
$$R = \left(\frac{1}{6} + \frac{1}{3} \right)^{-1} = \left(\frac{1}{2} \right)^{-1} = 2\Omega$$



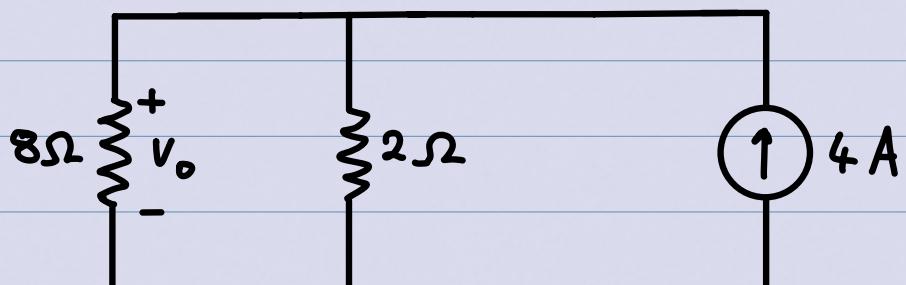Using superposition, we "turn off" the 2A C source:




we know the voltage drop across the 8Ω resistor and the 2Ω resistor must be the same.

$$\left(\frac{1}{8} + \frac{4}{8} \right)^{-1} = \frac{8}{5} = R_{eq}$$

$\rightarrow \frac{32}{5} V$ is dropped over the resistors

$$V_{drop} = i_o R \rightarrow V_{drop} = 4 \left(\frac{8}{5} \right) \rightarrow \frac{32}{5} .$$

now, we "turn off" the $4A$ C source:

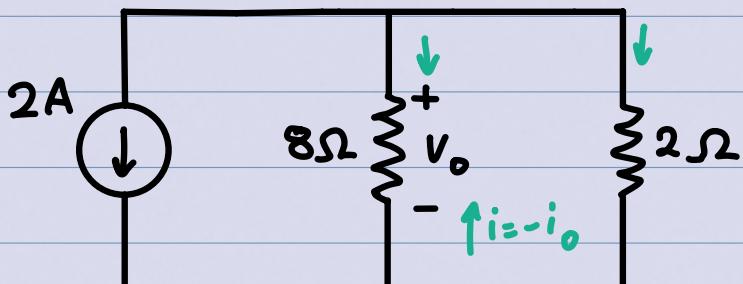

$$R_{eq} = \left(\frac{1}{8} + \frac{4}{8} \right)^{-1} = \frac{8}{5}$$



$$V_{drop} = i_o R_{eq} = 2 \left(\frac{8}{5} \right) = \frac{16}{5} .$$

since the $2A$ CS is pushing current up the resistors, we must subtract the V components!



$$\therefore \frac{32}{5} - \frac{16}{5} = \frac{16}{5} V$$

Thevenin's Theorem :

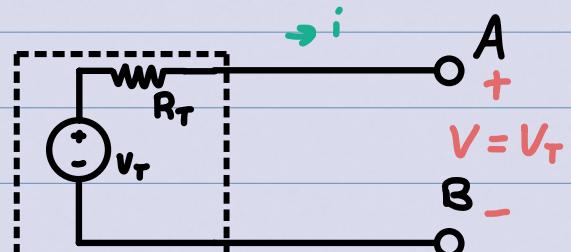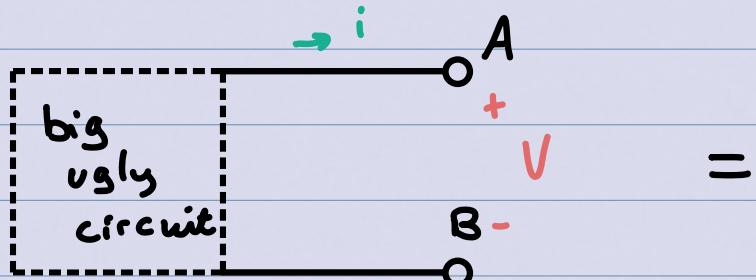* sorry, my notes don't have thevenin / norton!



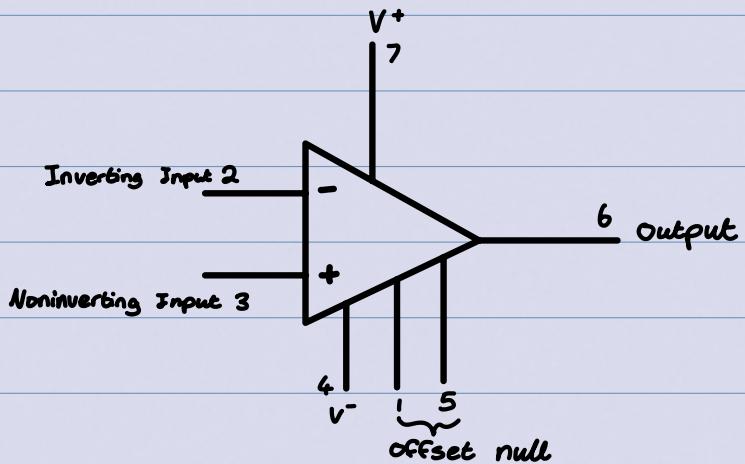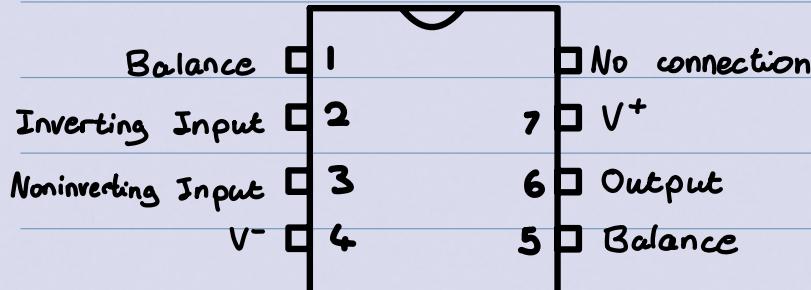Operational Amplifiers: a circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration.



More simply:


$$V_1 \xrightarrow{-} V_2 \xrightarrow{+} V_O \rightarrow V_O = A(V_1 - V_2)$$

op-amp's intrinsic multiplier!


In an ideal op-amp, both inputs should have equal voltage and 0 current!!!

Op-amp Circuit:

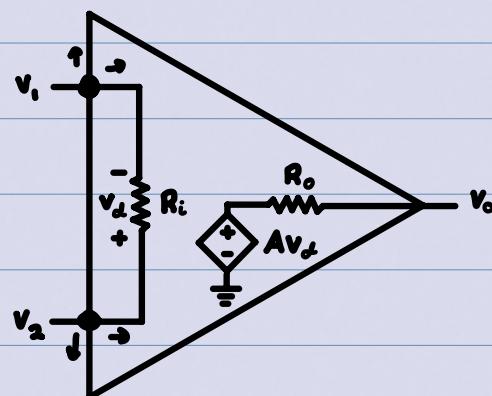
* to solve op-amp questions, just replace the op-amp with its circuit!



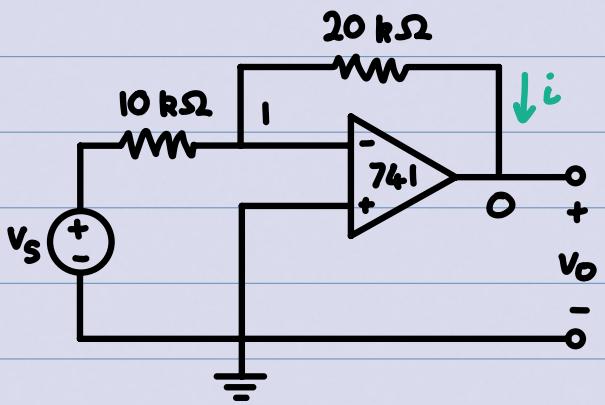Example: Find the closed-loop gain $\frac{V_o}{V_s}$ if the op-amp has an open-loop voltage gain of 2×10^5 , input resistance of $2 M\Omega$, and output resistance of 50Ω . The circuit is as follows:



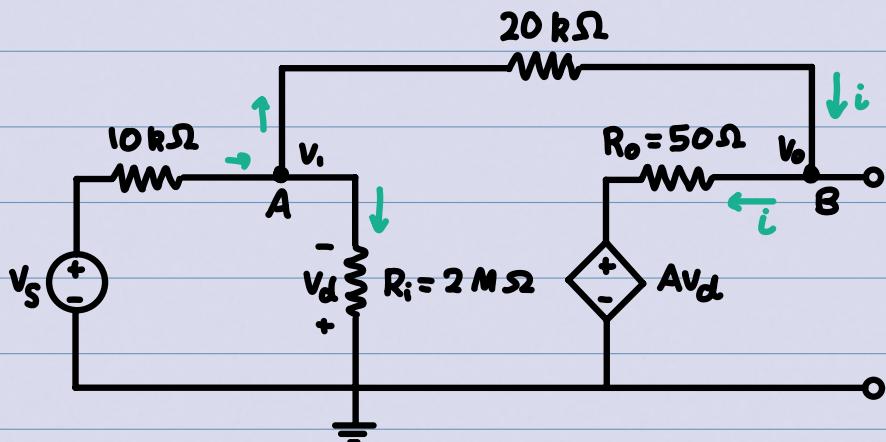The first step is to re-draw the circuit using the op-amp's internal circuit:



Now, we can use Nodal Analysis! At node A :

$$\hookrightarrow \text{KCL} : \frac{V_s - V_i}{10 \text{ k}\Omega} = \frac{V_i - V_o}{20 \text{ k}\Omega} + \frac{V_i}{2 \text{ M}\Omega}$$

$$\hookrightarrow \frac{V_s - V_i}{10 \cdot 10^3} = \frac{V_i - V_o}{20 \cdot 10^3} + \frac{V_i}{2 \cdot 10^6}$$

$$\hookrightarrow 2 \cdot 10^2 (V_s - V_i) = 10^2 (V_i - V_o) + V_i$$

$$\hookrightarrow \therefore 200 V_s - 200 V_i = 100 V_i - 100 V_o + V_i$$

$$\hookrightarrow 200 V_s = 301 V_i - 100 V_o \longrightarrow V_i = \frac{2 V_s + V_o}{3}$$

$$\text{At node B: } \frac{V_i - V_o}{20 \text{ k}\Omega} = \frac{V_o - AV_d}{50}$$

$$\rightarrow \frac{V_i - V_o}{20 \cdot 10^3} = \frac{V_o - A V_d}{50} \rightarrow V_i - V_o = 400(V_o - A V_d)$$

From the circuit, we see that $V_{cl} = -V_i$, and from the question, we see that $A = 2 \cdot 10^5 = 200,000$.

$$\therefore V_i - V_o = 400(V_o - A V_d) \rightarrow V_i - V_o = 400(V_o + 200000 V_i)$$

$$\text{Substituting: } \frac{2V_s + V_o}{3} - V_o = 400(V_o + 200000) \frac{2V_s + V_o}{3}$$

$$\hookrightarrow 2V_s + V_o - 3V_o = 1200(V_o + 200000) \frac{2V_s + V_o}{3}$$

$$\hookrightarrow 2V_s - 2V_o = 1200V_o + 2400000000 \frac{2V_s + V_o}{3}$$

$$\hookrightarrow 2V_s - 2V_o = 1200V_o + \frac{4800000000}{3}V_s + \frac{2400000000}{3}V_o$$

$$\hookrightarrow 2V_s - 2V_o = 1200V_o + 1600000000V_s + 80000000V_o$$

$$\hookrightarrow 2V_s - 2V_o = 1600000000V_s + 80001200V_o$$

$$\hookrightarrow 160000002V_s = -80001202V_o$$

$$\hookrightarrow \frac{V_o}{V_s} = -1.9999699.$$

\therefore the closed-loop gain $\frac{V_o}{V_s} = -1.9999699!$


Ideal Op-Amp: an amplifier with infinite open-loop gain, infinite input resistance, and

zero output resistance.

↳ ie, $A \approx \infty$, $R_i \approx \infty$, and $R_o \approx 0$.

↳ since the input resistance is ∞ , there should be no current entering an ideal op-amp!
Also, the inputs should have an equal voltage!

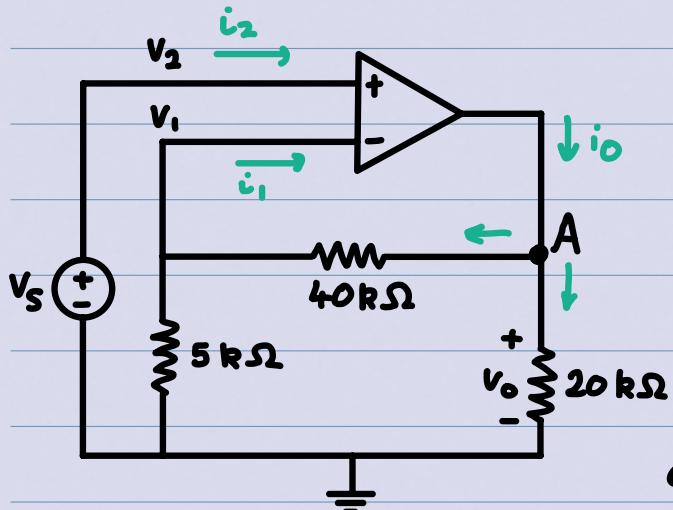Example: find the closed-loop gain of the ideal op-amp in the following circuit:



- Since the op-amp is ideal, we know that $i_1 = i_2 = 0$!
- We also know that $V_1 = V_2 = V_s$!
- Since $i_1 = 0$, all of the current that goes through the $40\text{k}\Omega$ resistor also goes through the $5\text{k}\Omega$ resistor.

∴, the $40\text{k}\Omega$ and $5\text{k}\Omega$ resistors are in series!

from the voltage divider principle, we see that:


$$V_1 = V_o \frac{5}{40+5}$$

$$\hookrightarrow V_1 = \frac{V_o}{9} \rightarrow V_o = 9V_1 !$$

Since we saw that $V_1 = V_2 = V_s$, $V_o = 9V_s \rightarrow \frac{V_o}{V_s} = 9$.

\therefore the closed-loop gain $\frac{V_o}{V_s}$ is 9.

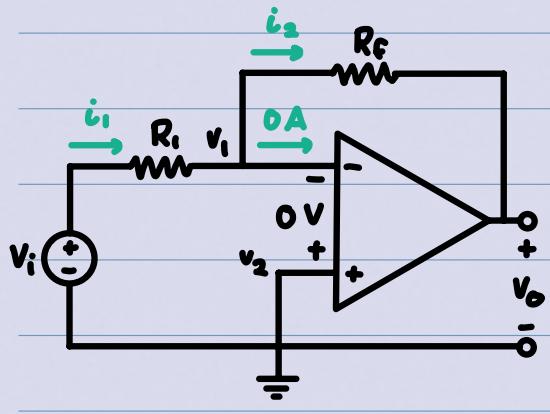Inverting Amplifier: Noninverting input is grounded, V_i is connected to the inverting input through R_i , and the feedback resistor R_f is connected between the inverting input and output.




- An inverting amplifier reverses the polarity of the input signal while amplifying it.

$$\rightarrow * V_o = - \frac{R_f}{R_i} V_i$$

Note: V_o depends only on R_f and R_i , which are external factors to the amplifier!

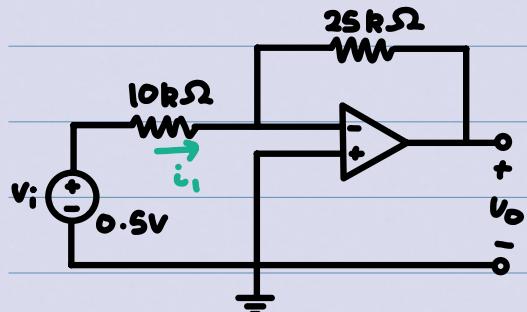Example: find the output voltage V_o and the current i_i in the $10\text{ k}\Omega$ resistor in the circuit:




note that $R_f = 25\text{ k}\Omega$ and $R_i = 10\text{ k}\Omega$. Then, we simply apply the inverting amplifier eq.

$$\rightarrow V_o = - \frac{R_f}{R_i} = - \frac{25\text{ k}\Omega}{10\text{ k}\Omega} \rightarrow V_o = - \frac{5}{2} V.$$

$$i_i = \frac{V_i - 0}{R_i} = \frac{0.5 V}{10\text{ k}\Omega} \rightarrow i_i = 50 \mu A.$$

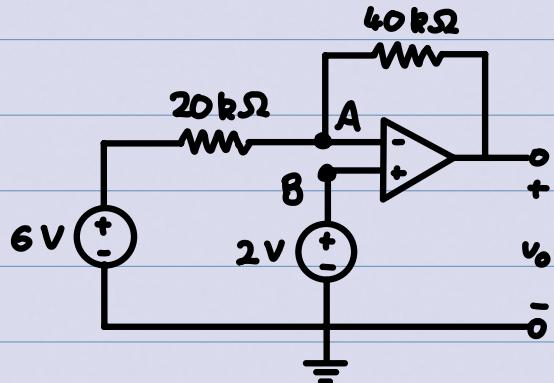Example: determine V_o in the op-amp circuit:



KCL at node A:


$$\rightarrow \frac{6 - V_A}{20 \cdot 10^3} = \frac{V_A - V_o}{40 \cdot 10^3}$$

$$\hookrightarrow V_o = 3V_A - 12.$$

Since we are dealing with ideal op-amps, we know $V_A = V_B$. Since $V_B = 2$, $V_A = 2$.

$$\therefore V_o = 3(2) - 12 = -6 \text{ V.}$$

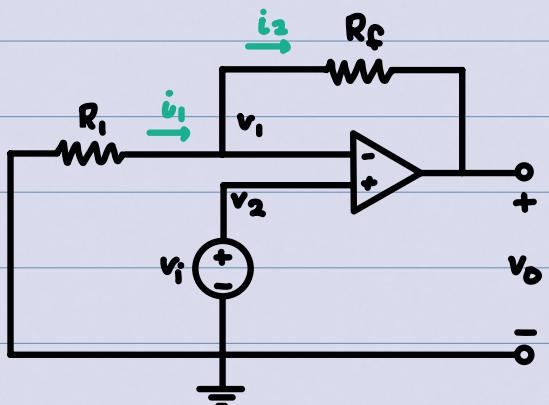Noninverting Amplifier: the input voltage v_i is applied directly at the noninverting input terminal, and R_i is connected between the ground and the inverting terminal.



- A noninverting amplifier is an op-amp circuit designed to provide a positive voltage gain.


$$* V_o = V_i \left(\frac{R_f}{R_i} + 1 \right)$$

Note: like an inverting amplifier, a noninverting amplifier's gain only depends on external factors.

If $R_f = 0$ or $R_i = \infty$, the gain becomes 1, so

$$V_o = V_i !$$

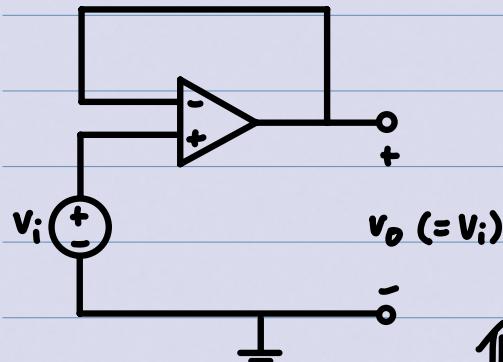
↳ this would simplify the circuit as such:



• This is called a **voltage follower!**
 ↳ $V_o = V_i$ for a voltage follower.

These are usually just used as buffers.

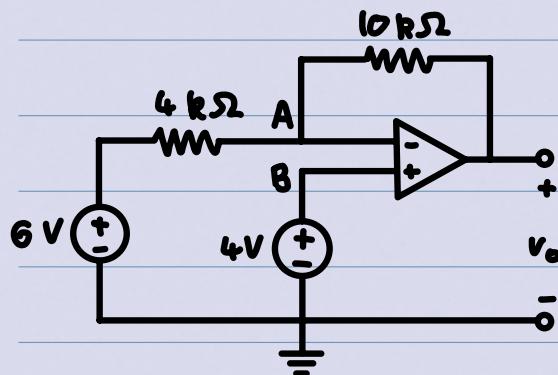Example: find the output voltage V_o in the circuit.



KCL at node A :

$$\frac{6 - V_A}{4 \cdot 10^3} = \frac{V_A - V_o}{10 \cdot 10^3}$$


we know $V_A = V_B$ as the op-amp is ideal.

since $V_B = 4$, V_A must be 4. $\rightarrow V_A = 4$.


$$\therefore \frac{6 - (4)}{4 \cdot 10^3} = \frac{(4) - V_o}{10 \cdot 10^3} \rightarrow \frac{2}{4} = \frac{4 - V_o}{10} \rightarrow 5 = 4 - V_o$$

$$\hookrightarrow \therefore V_o = -1 \text{ V.}$$

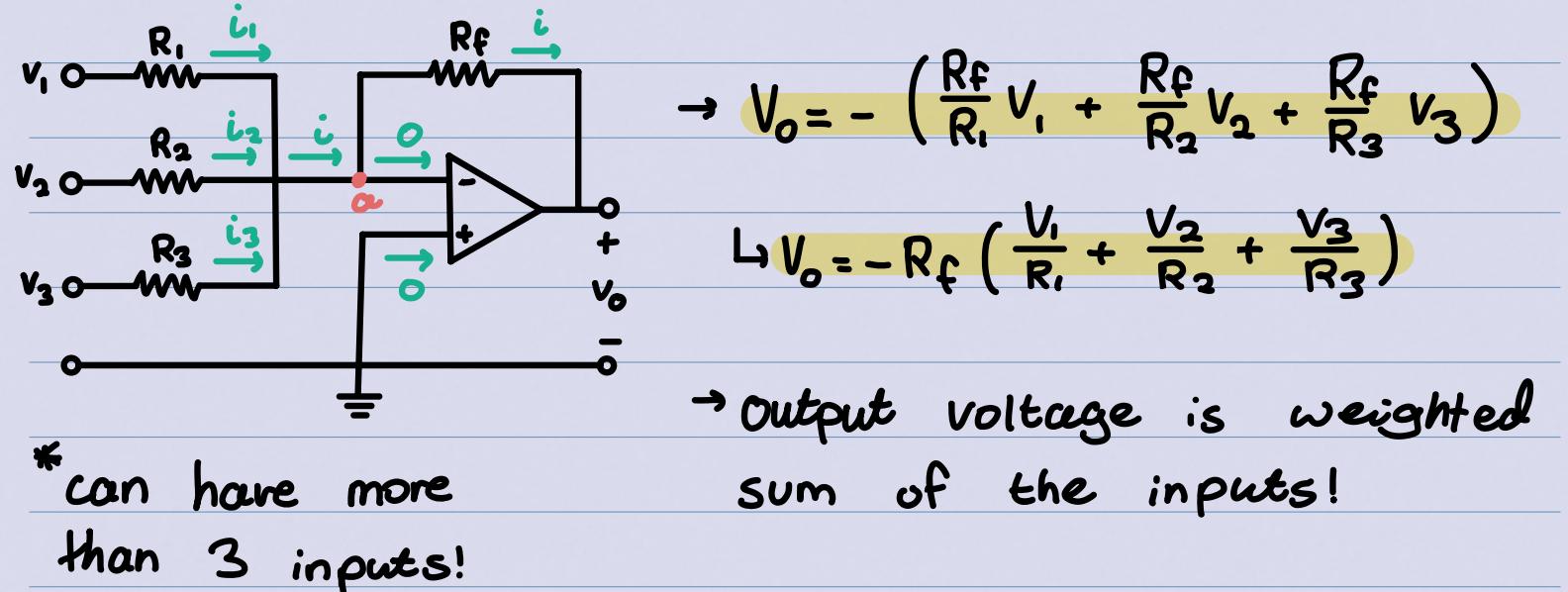Summing Amplifier: an op-amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.



Example: Calculate V_o and i_o :

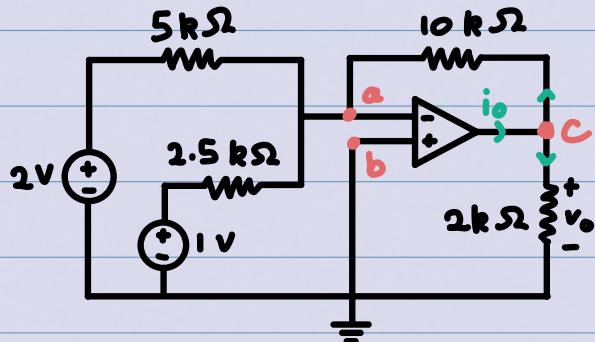

Note that this is very similar to the summing circuit above, only it has 2 inputs instead of 3.

from the summing amplifier circuit, $V_o = -10 \left(\frac{2}{5} + \frac{1}{2.5} \right)$

$$\hookrightarrow V_o = -10 \left(\frac{4}{5} \right) = -8 \text{ V.}$$

KCL at node C: $i_o = \frac{V_o - V_a}{10} + \frac{V_o - 0}{2}$.


since $V_b = 0$, and since this is an ideal op-amp, we know $V_a = V_b$, so $V_a = 0$.

$$\hookrightarrow i_o = \frac{V_o}{10} + \frac{V_o}{2} = -\frac{8}{10} - 4 = -4.8 \text{ mA}$$

mA bc resistors are $\text{k}\Omega$, not Ω .

Difference Amplifier: a device that amplifies

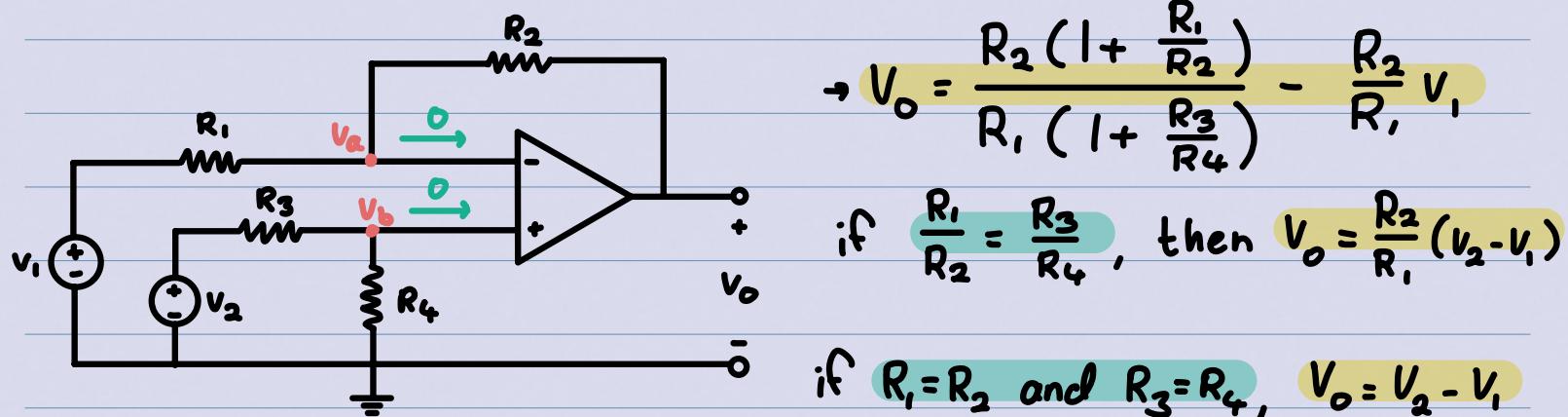the difference between two inputs but rejects any signals common to the two inputs.



Example: design a circuit with inputs V_1 and V_2 such that $V_0 = 3V_2 - 5V_1$.

from the general difference amplifier equation, we see that $\frac{R_2}{R_1} = 5 \rightarrow R_2 = 5R_1$.


$$\therefore 5 \frac{(1 + \frac{R_1}{R_2})}{(1 + \frac{R_3}{R_4})} = 3 \rightarrow \frac{1 + (5)^{-1}}{1 + \frac{R_3}{R_4}} = \frac{3}{5}$$

$$\hookrightarrow \frac{6/5}{1 + \frac{R_3}{R_4}} = \frac{3}{5} \rightarrow 2 = 1 + \frac{R_3}{R_4} \rightarrow \frac{R_3}{R_4} = 1 \rightarrow R_3 = R_4$$


$$\therefore R_2 = 5R_1 \text{ and } R_3 = R_4$$

let's choose $R_1 = 10\Omega$ and $R_3 = 20\Omega$, then $R_2 = 50\Omega$ and $R_4 = 20\Omega$.

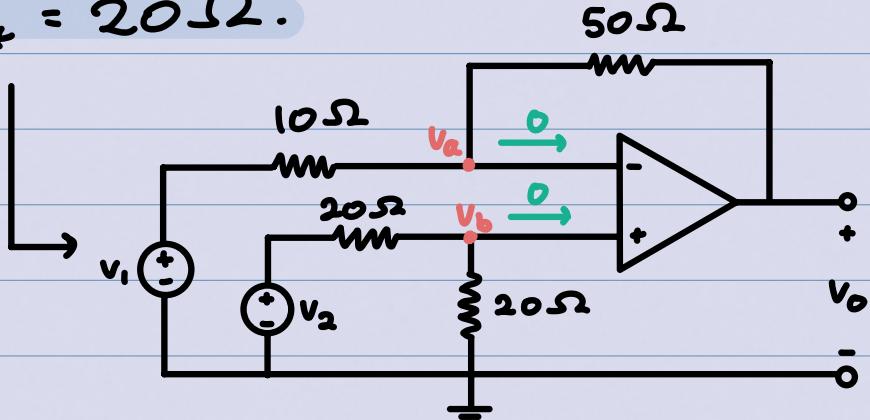note: this problem can also be solved using cascading op-amps!



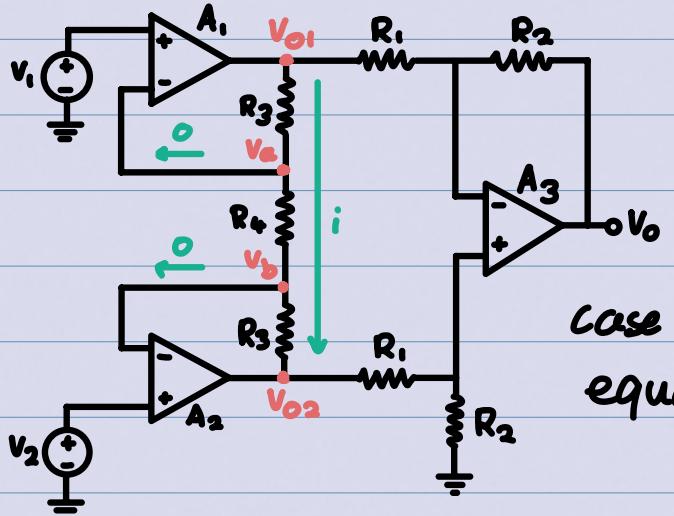Example: show that $V_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4}\right) (V_2 - V_1)$ in the following circuit:



- we recognise that A_3 is a difference amplifier!

- this falls into the second

case given in the difference amplifier equations, and hence $V_o = \frac{R_2}{R_1} (V_{02} - V_{01})$

Since op-amps A_1 and A_2 are ideal, they take in 0 current.

$\hookrightarrow \therefore R_3, R_4$, and the other R_3 are in series!

$$i = \frac{V_{02} - V_{01}}{R_3 + R_4 + R_3} \rightarrow V_{02} - V_{01} = (2R_3 + R_4)i$$

also, $i = \frac{V_a - V_b}{R_4}$, and $V_a = V_1$ and $V_b = V_2$.


$$\hookrightarrow \therefore i = \frac{V_1 - V_2}{R_4}$$

$$V_o = \frac{R_2}{R_1} (V_{02} - V_{01}) \rightarrow V_o = \frac{R_2}{R_1} i (2R_3 + R_4)$$


$$\hookrightarrow V_o = \frac{R_2}{R_1} \frac{V_1 - V_2}{R_4} (2R_3 + R_4) \rightarrow V_o = \frac{R_2}{R_1} (V_1 - V_2) \left(\frac{2R_3}{R_4} + 1\right)$$

Cascaded Op-Amp Circuits: a head-to-tail arrangement of two or more op-amp circuits such that the output of one is the input of the other

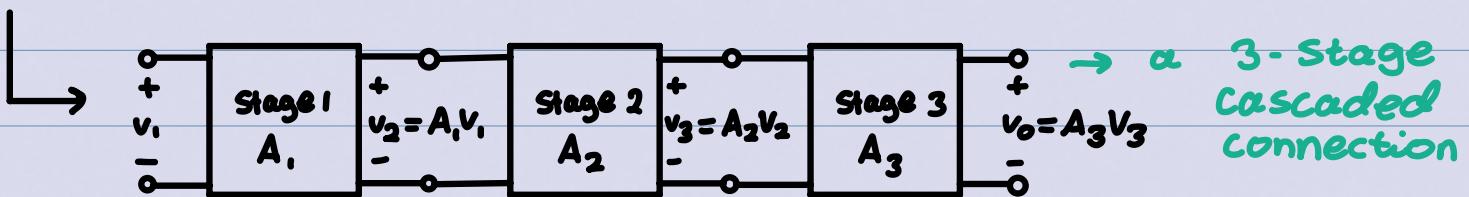→ when op-amp circuits are cascaded, each circuit in the string is called a stage.



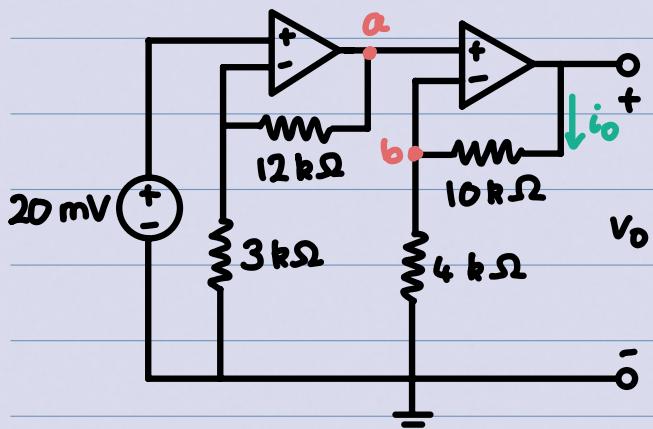Example: find V_o and i_o in the following circuit:




notice that this is just two noninverting amplifiers cascaded!

↳ can use: $V_o = V_i \left(\frac{R_f}{R_i} + 1 \right)$

↳ we see that $V_a = 20 \left(\frac{12}{3} + 1 \right) = 100 \text{ mV}$.

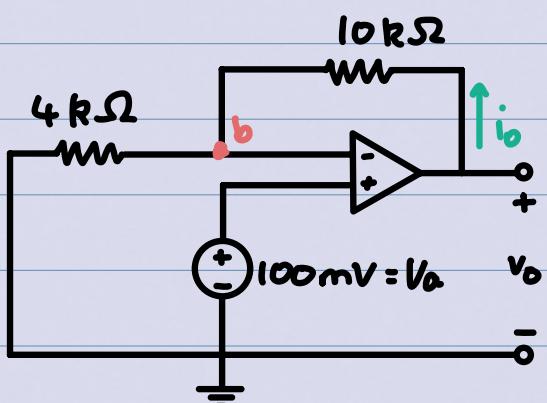now, we can re-draw the circuit to simplify:



→ now, it's clear that

$$V_o = V_a \left(\frac{10}{4} + 1 \right)$$

$$V_o = 100 \left(3.5 \right) = 350 \text{ mV.}$$

we see that i_o goes through the $10 \text{ k}\Omega$ resistor:

↳ $i_o = \frac{V_o - V_b}{10 \text{ k}\Omega} = \frac{V_o - V_a}{10 \text{ k}\Omega} = \frac{350 \text{ mV} - 100 \text{ mV}}{10 \text{ k}\Omega} = 25 \mu\text{A.}$

Capacitors: two conducting plates separated by

an insulator (or dielectric).

Capacitance: the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates.


$$\hookrightarrow C = \frac{Q}{V} \quad [F]$$

→ from $i = \frac{dq}{dt}$, we see that $i = C \frac{dv}{dt}$.


the energy stored on a capacitor is $W = \frac{1}{2} CV^2$.
↳ stored in the electric field

- A capacitor is an open-circuit to DC
- The voltage on a capacitor cannot change abruptly.

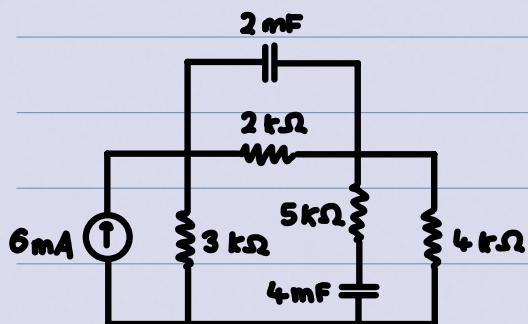Example: find the energy stored in each capacitor




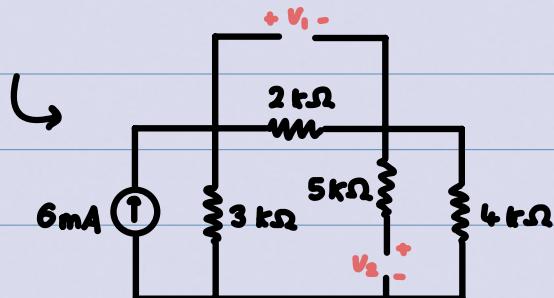• Under dc conditions, we replace each capacitor with an open circuit!




→ we see that no current flows the top loop or the 5kΩ resistor!
∴, the 2 and 4 kΩ resistors are in parallel!

we can re-draw again for clarity:

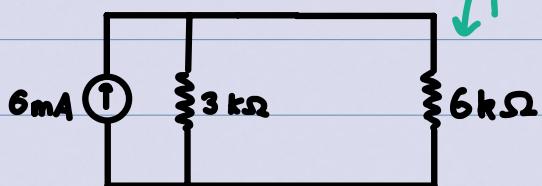

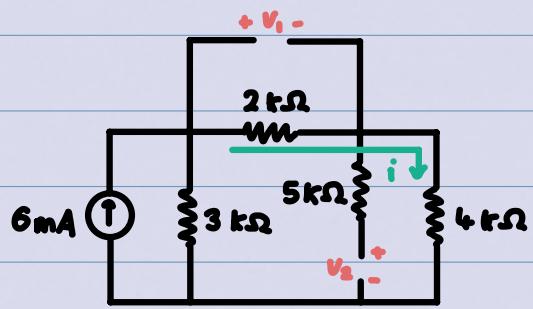→ from here, we can see that
 $i = 2 \text{ mA}$.



$$\therefore V_1 = 2000; \text{ and } V_2 = 4000;$$

$$\hookrightarrow V_1 = 4V, \text{ and } V_2 = 8V.$$


$$\omega_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (2 \cdot 10^{-3})(4^2) = 16 \text{ mJ}$$

$$\omega_2 = \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (4 \cdot 10^{-3})(8^2) = 128 \text{ mJ}.$$


Series and parallel Capacitors:

- The equivalent capacitance of N parallel capacitors is the sum of the individual capacitances $\rightarrow C_{eq} = C_1 + C_2 + \dots + C_n$
- The equivalent capacitance of N series capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances $\rightarrow C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)^{-1}$

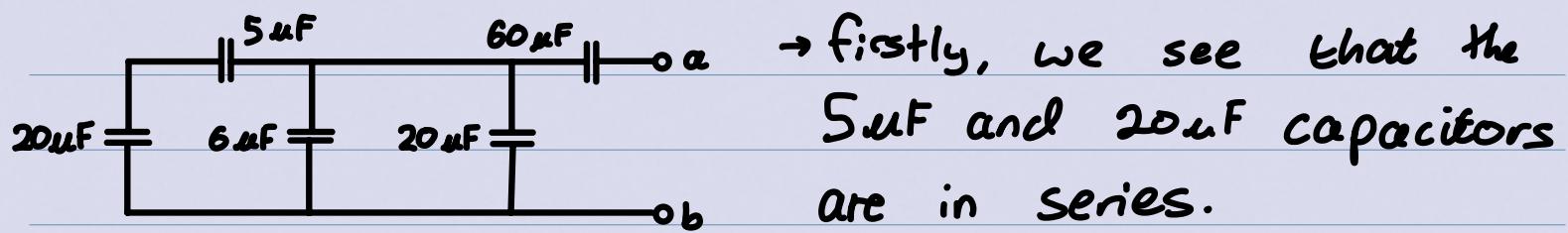Example: find the equivalent capacitance seen between the terminals a and b in the following circuit:



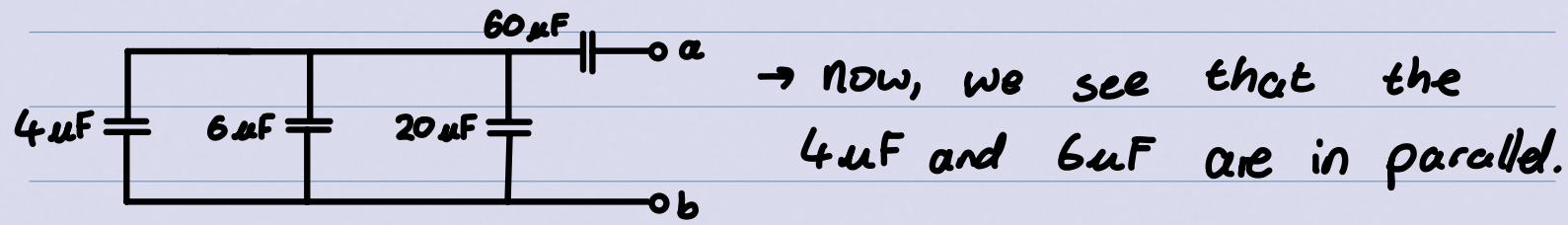
$$\therefore R_{20,5} = \left(\frac{1}{5} + \frac{1}{20} \right)^{-1} = \left(\frac{5}{20} \right)^{-1} = 4 \mu\text{F}.$$



$$\therefore R_{4,6} = 4 + 6 = 10 \mu\text{F}.$$



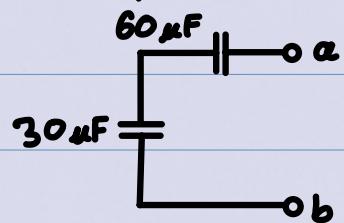
$$R_{10,20} = 10 + 20 = 30 \mu\text{F}.$$



→ again, the 10μF and 20μF capacitors are in parallel!

$$R_{\text{eq}} = \left(\frac{1}{30} + \frac{1}{60} \right)^{-1} = \left(\frac{3}{60} \right)^{-1} = 20 \mu\text{F} !$$

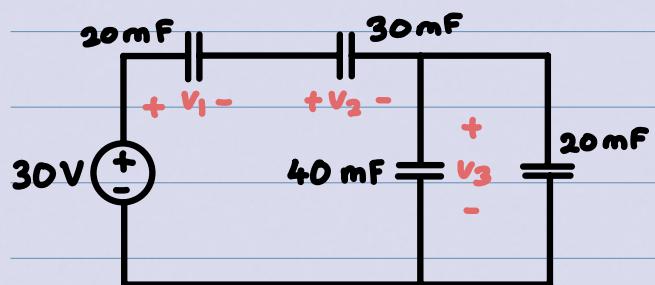Example: find the voltage across each capacitor:



→ let's first find the equivalent capacitance C_{eq} :

$$C_{\text{eq}} = \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{40} \right)^{-1}$$

$\hookrightarrow C_{\text{eq}} = 10 \text{ mF}.$

\therefore the total charge is $q = C_{eq}V \rightarrow q = (10 \cdot 10^{-3})(30)$
 $\hookrightarrow q = 0.3 \text{ C.}$

this is the charge on the 20mF and 30mF capacitors, as they are in series with the 30V source:

$$\therefore V_1 = \frac{q}{C_1} = \frac{0.3}{20 \cdot 10^{-3}} = 15 \text{ V}$$

$$V_2 = \frac{q}{C_2} = \frac{0.3}{30 \cdot 10^{-3}} = 10 \text{ V.}$$

we can now perform KVL: $-30 + V_1 + V_2 + V_3 = 0$
 $\hookrightarrow V_3 = 30 - V_1 - V_2 = 5 \text{ V.}$

Inductors: a coil of conducting wire

Inductance: the property whereby an inductor exhibits opposition to the change of current flowing through it.

\hookrightarrow the voltage across an inductor is $V = L \frac{di}{dt}$.

the energy stored by an inductor is $\omega = \frac{1}{2} Li^2$!

- An inductor acts like a short circuit to dc
- The current flowing through an inductor cannot change instantaneously.


Example: the current through a 0.1H inductor is $i(t) = 10te^{-5t}$. Find the voltage across the inductor and the energy stored by it.

$$\hookrightarrow v = L \frac{di}{dt} = (0.1) \frac{d}{dt} (10te^{-5t}) = e^{-5t} + t(-5)e^{-5t}$$


$$\hookrightarrow V = e^{-5t}(1 - 5t) \text{ V}$$

$$\omega = \frac{1}{2} Li^2 = \frac{1}{2} (0.1) (10te^{-5t})^2 = 5t^2 e^{-10t} \text{ J.}$$

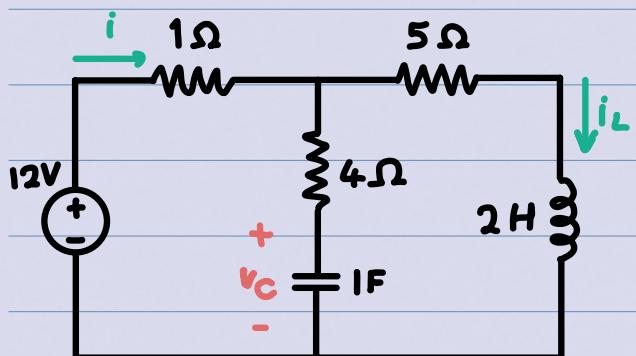Example: Find (a) i , V_C , i_L , and (b), the energy stored in the capacitor and inductor:



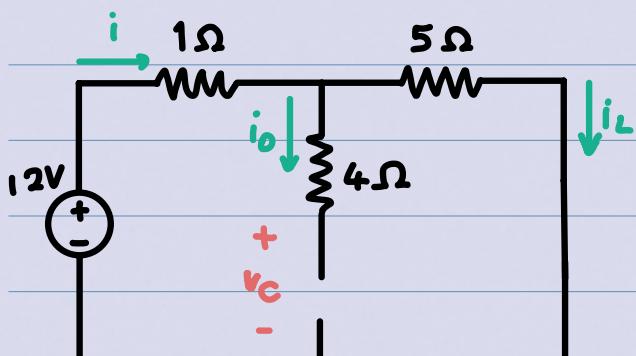→ we replace the capacitor with an open-circuit and the inductor with a short-circuit as follows:



→ since no current flows through the 4Ω resistor, the 1Ω and 5Ω resistors are in series.

$$\hookrightarrow i = \frac{V}{R} = \frac{12}{5+1} = 2 \text{ A} = i_L$$

the voltage V_C is the same as the voltage across

the 5Ω resistor

$$\hookrightarrow V_C = 5i = 5(2) = 10 \text{ V.}$$

$$\omega_C = \frac{1}{2} CV_C^2 = \frac{1}{2} (1)(10)^2 = 50 \text{ J}$$


$$\omega_L = \frac{1}{2} L i^2 = \frac{1}{2} (2)(2)^2 = 4 \text{ J}$$

Series and Parallel Inductors

the equivalent inductance of series inductors is the sum of their individual inductances. $\rightarrow L_{eq} = L_1 + L_2 + \dots + L_N$

the equivalent inductance of parallel inductors is the reciprocal of the sum of the reciprocals of the individual inductances. $\rightarrow L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right)^{-1}$

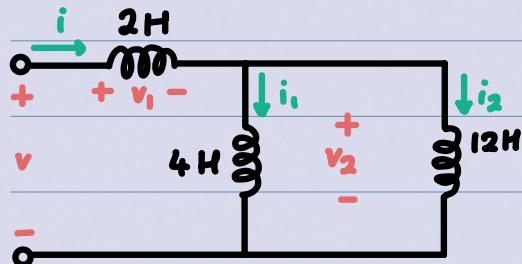Example: $i(t) = 4(2 - e^{-10t})$ mA. If $i_2(0) = -1$ mA, find: (a) $i_1(0)$, (b) $v(t)$, $v_1(t)$, and $v_2(t)$, and (c) $i_1(t)$ and $i_2(t)$:



\rightarrow we see that $i = i_1 + i_2$.

$$\therefore i(0) = i_1(0) + i_2(0)$$

$$\hookrightarrow 4 = i_1(0) - 1 \rightarrow i_1(0) = 5 \text{ mA}$$

(a)

$$L_{eq} = 2 + \left(\frac{1}{4} + \frac{1}{12} \right)^{-1} = 2 + \left(\frac{4}{12} \right)^{-1} = 5 \text{ H.}$$

$$v(t) = L_{eq} \frac{di}{dt} = 5(4)(-1)(-10)e^{-10t} \text{ mV}$$

$$\hookrightarrow v(t) = 200e^{-10t} \text{ mV}$$

$$V_i(t) = L \frac{di}{dt} = 2(4)(-1)(-10)e^{-10t} \text{ mV}$$

$$\hookrightarrow V_i(t) = 80e^{-10t} \text{ mV}$$

$$V = V_1 + V_2 \rightarrow V_2(t) = V(t) - V_i(t) = 120e^{-10t} \text{ mV}$$

$$V = L \frac{di_1}{dt} \rightarrow di_1 = \frac{V_2}{L_1} dt \rightarrow i_1 = \frac{1}{L_1} \int V_2 dt + i_1(0)$$

$$\hookrightarrow i_1 = \frac{1}{4} \int 80e^{-10t} dt + 5 \text{ mA}$$


$$\hookrightarrow i_1 = 8 - 3e^{-10t} \text{ mA}$$

$$V = L \frac{di_2}{dt} \rightarrow di_2 = \frac{V_2}{L_2} dt \rightarrow i_2 = \frac{1}{L_2} \int V_2 dt + i_2(0)$$

$$\hookrightarrow i_2 = \frac{1}{12} \int 120e^{-10t} dt - 1 \text{ mA}$$

$$\hookrightarrow i_2 = -e^{-10t} \text{ mA}$$

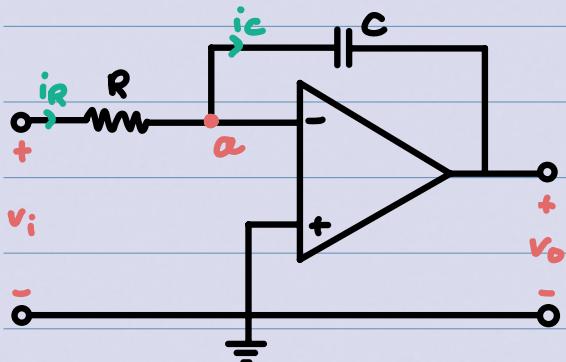
Integrator: an op-amp circuit whose output is proportional to the integral of the input signal.



→ note that this is simply an inverting amplifier, but the feedback resistor is replaced with a capacitor.

$$\hookrightarrow \text{assuming } V_o(0) = 0, V_o = -\frac{1}{RC} \int_0^t V_i(t) dt$$

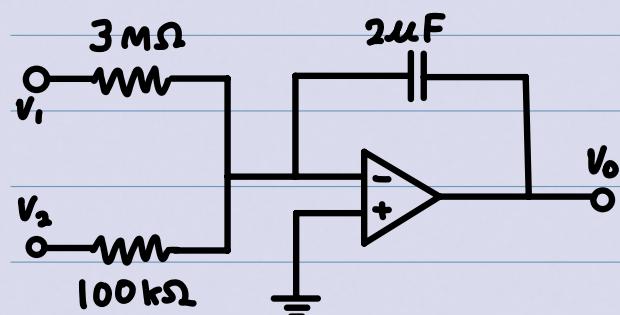Example: if $V_1 = 10 \cos(2t)$ mV and $V_2 = 0.5t$ mV, find V_o in the op-amp circuit. Assume the voltage across the capacitor is initially 0.



$$\rightarrow V_i = V_1 + V_2 .$$


$$\text{we know } V_o = -\frac{1}{RC} \int_0^t V_i(t) dt$$

$$\therefore V_o = -\frac{1}{R.C} \int_0^t V_1 dt - \frac{1}{R_2 C} \int_0^t V_2 dt$$

$$= -\frac{1}{3 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 10 \cos(2t) dt - \frac{1}{100 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 0.5t dt$$

$$\hookrightarrow V_o = -0.833 \sin(2t) - 1.25t^2 \text{ mV}$$

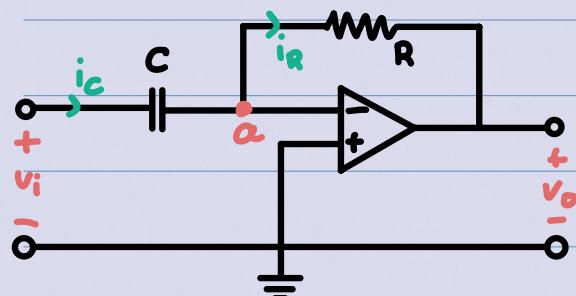Differentiator: an op-amp circuit whose **output** is proportional to the **rate of change** of the input.




→ note that this is also just the **inverting amplifier**, but the **input resistor** is replaced with a **capacitor**.


$$\hookrightarrow V_o = -RC \frac{dV_i}{dt}$$

↳ The differentiator is rarely used in practice; it's not as accurate as the integrator.

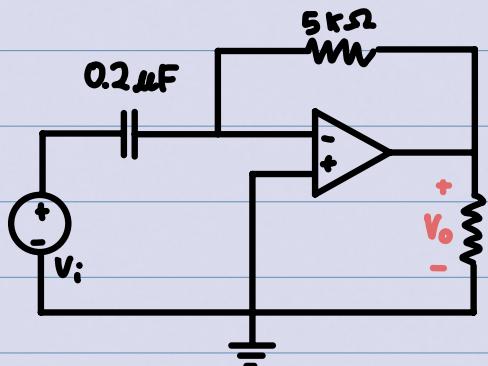Example: Sketch the output voltage for the circuit, given the input voltage. Assume $V_o(0) = 0$.



input voltage V_i :

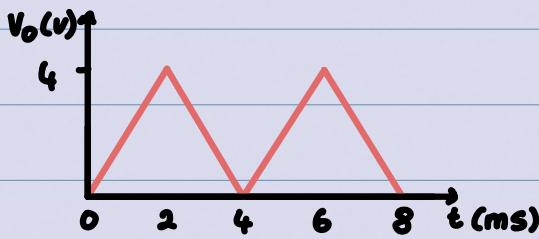

this is a differentiator with $RC = 5 \cdot 10^3 \cdot \frac{2}{10} \cdot 10^{-6}$
 $\hookrightarrow RC = 10^{-3}$.

We can express V_i as:

$$\left\{ \begin{array}{ll} 2000t & 0 < t < 2 \\ -2000t & 2 < t < 4 \\ 2000t & 4 < t < 6 \\ -2000t & 6 < t < 8 \end{array} \right\} .$$

\therefore , the output is obtained as $V_o = -RC \frac{dV_i}{dt}$

$$\hookrightarrow V_o = -10^{-3} \left\{ \begin{array}{ll} 2000 & 0 < t < 2 \\ -2000 & 2 < t < 4 \\ 2000 & 4 < t < 6 \\ -2000 & 6 < t < 8 \end{array} \right\} .$$

$$\hookrightarrow \therefore V_o = \left\{ \begin{array}{ll} -2 & 0 < t < 2 \\ 2 & 2 < t < 4 \\ -2 & 4 < t < 6 \\ 2 & 6 < t < 8 \end{array} \right\} V.$$

First-order circuit: characterized by a first-order differential equation.


Source-Free RC circuit: occurs when the source of a circuit with a resistor and capacitor is suddenly disconnected.

Time Constant (τ) = the time required for the response to decay a factor of $1/e$ (or 36.8%)

of its initial value.

For an RC circuit, $V = V_0 e^{-t/\tau}$, and $\tau = RC$

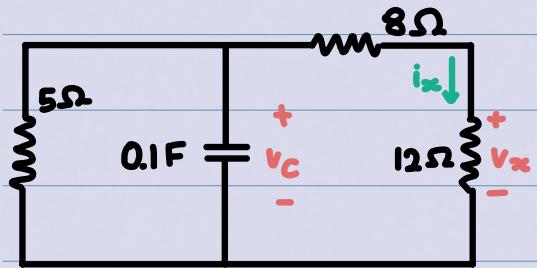Example: let $V_C(0) = 15V$. Find V_C , V_x , and i_x if $t > 0$:



the 8Ω and 12Ω resistor can be combined into a 20Ω resistor, as they're in Series.

Then, the 5Ω and 20Ω resistor are parallel, so $R_{eq} = \left(\frac{1}{5} + \frac{1}{20}\right)^{-1} = 4\Omega$.

$$T = R_{eq} C = 4 \cdot 0.1 = 0.4.$$


$$\hookrightarrow \therefore V_C = V = V_C(0) e^{-t/\tau} = 15 e^{-2.5t} V$$

We can use voltage division to find V_x :


$$\hookrightarrow V_x = \frac{12}{12+8} V = \frac{12}{20} V = \frac{3}{5} V = 9 e^{-2.5t} V.$$

$$i_x: \frac{V_x}{R_{12}} = \frac{9 e^{-2.5t}}{12} = \frac{3}{4} e^{-2.5t}.$$

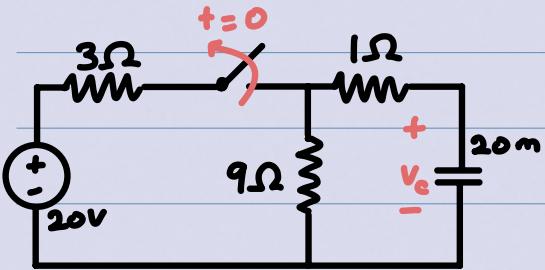Example: the switch has been closed for a long time and is opened at $t=0$. Find $v(t)$ for $t \geq 0$. Also, calculate the initial energy stored in the capacitor.




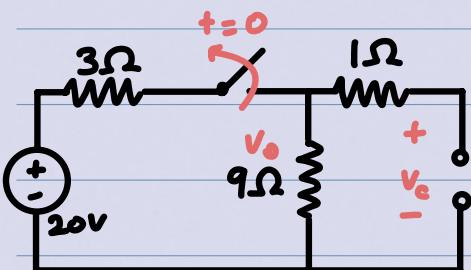as the capacitor acts like an open circuit after a long time ($t < 0$), we can find $V_c(0)$:



using voltage division, $V_0 = \frac{q}{q+3} (20) = V_c$.
 $\hookrightarrow V_c = 15 \text{ V}$ at $t \leq 0$. $\therefore V_c(0) = 15 \text{ V}$.

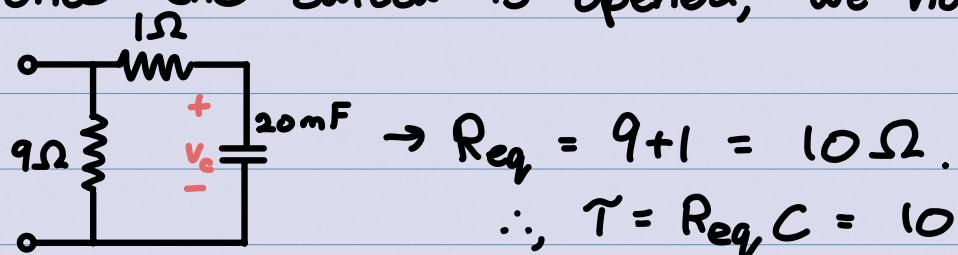once the switch is opened, we have this RC circuit:



$$\rightarrow R_{eq} = 9 + 1 = 10 \Omega.$$

$$\therefore T = R_{eq} C = 10 (20 \cdot 10^{-3}) = 0.2 \text{ s}$$

$$V_c(t) = V_c(0) e^{-t/T} = 15 e^{-5t} \text{ V.}$$

^{initial}
 The "energy stored in the capacitor is given by:


$$\hookrightarrow w_c(0) = \frac{1}{2} C V_c^2 = \frac{1}{2} (20 \cdot 10^{-3}) (15)^2 = 2.25 \text{ J.}$$

Source - Free RL circuit: occurs when the source of a circuit with a resistor and inductor is suddenly disconnected.

For an LR circuit, $T = \frac{L}{R}$ and $i(t) = I_0 e^{-t/T}$


Example: the switch in the circuit has been closed for a long time. At $t=0$, the switch is

opened. Calculate $i(t)$ for $t > 0$.

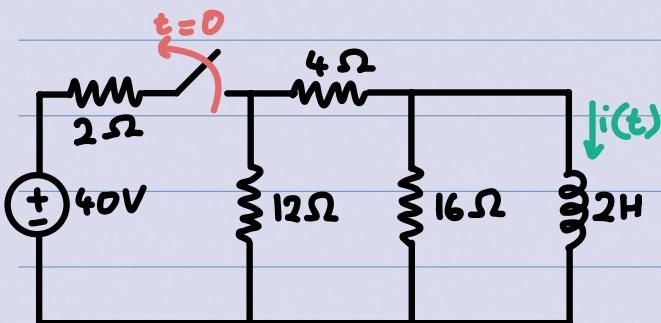

after a long time ($t < 0$),
the inductor acts as a
closed switch (wire).

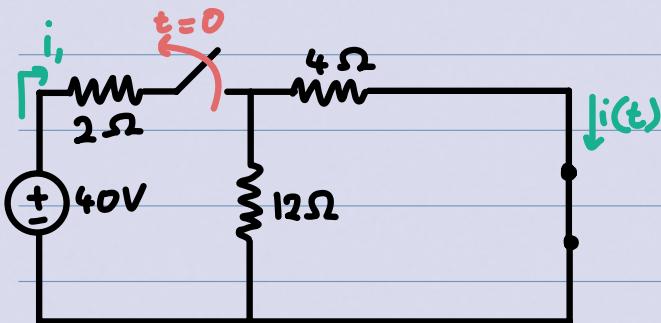This would result in the 16Ω resistor being short-circuited:



using the current divider rule,
 $i(t) = i_1 \frac{12}{12+4} = \frac{3}{4} i_1$.


we also see that $R_{eq} = 2 + \frac{48}{16} = 5\Omega$

$$\therefore i_1 = \frac{40V}{5\Omega} = 8A.$$

$$\hookrightarrow i(0) = 8 \left(\frac{3}{4}\right) = 6A.$$

Since current cannot instantaneously change in an inductor, $I(0) = I(0^-)$.

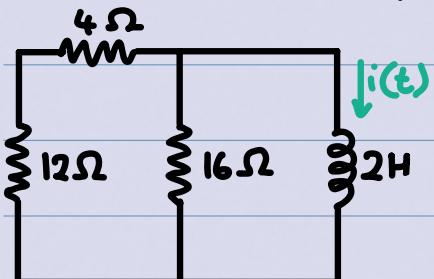when the switch is opened, the inductor will act as the new power source:



$$R_{eq} = 8\Omega. \therefore \tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4}.$$

$$\therefore i(t) = i_0 e^{-t/\tau} = 6e^{-4t} A.$$

Singularity Functions: functions that are either discontinuous or have discontinuous derivatives.

the unit step function $u(t)$ is 0 for negative values

of t and 1 for positive values of t .

$$\hookrightarrow u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases} \rightarrow u(0) \text{ is undefined!}$$

$$\hookrightarrow \therefore v(t) = \begin{cases} 0, & t < t_0 \\ 1, & t \geq t_0 \end{cases} \text{ can be expressed as } v(t) = V_0 u(t - t_0).$$

the unit impulse function $\delta(t)$ is 0 everywhere except at $t=0$, where it is undefined.


$$\hookrightarrow \int_{0^-}^{0^+} \delta(t) dt = 1 \longrightarrow \therefore f(t_0) = \int_a^b f(t) \delta(t - t_0) dt$$

the unit ramp function $r(t)$ is 0 for negative values of t and has a unit slope for positive t .


$$\hookrightarrow r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}, \quad r(t - t_0) = \begin{cases} 0, & t \leq t_0 \\ t - t_0, & t \geq t_0 \end{cases}$$

$$\frac{dr(t)}{dt} = u(t), \quad \frac{du(t)}{dt} = \delta(t)$$

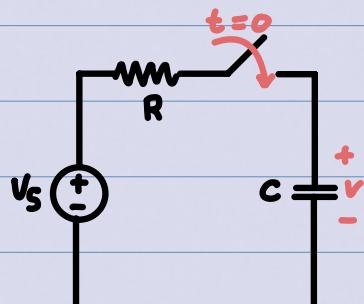Step Response of an RC circuit: the behavior when the excitation is the step function, which may be a voltage or current source.



→ can be redrawn as →

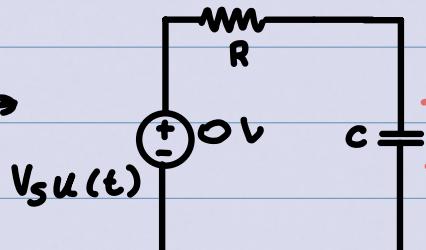


$$\hookrightarrow V(t) = \begin{cases} V_0 & , t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} & , t > 0 \end{cases}$$

transient response: the circuit's temporary response that will die out with time.


the steady state response: the circuit's long-term behavior after external excitation is applied.

$$\hookrightarrow V(t) = V(\infty) + [v(0) - V(\infty)]e^{-\frac{t}{\tau}}$$

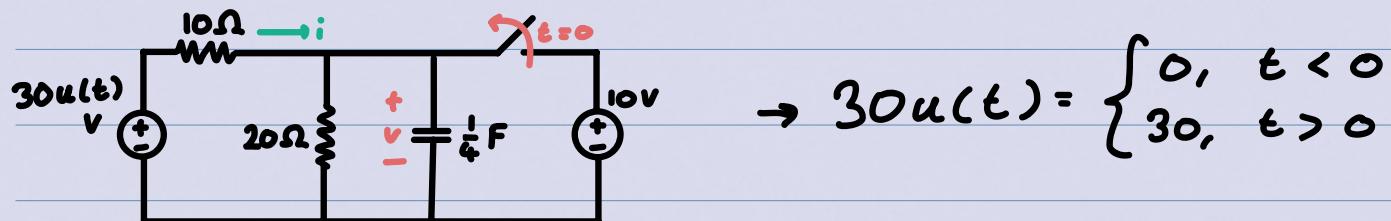
Example: the switch has been closed for a long time and is opened at $t=0$. Find i and v for all time.



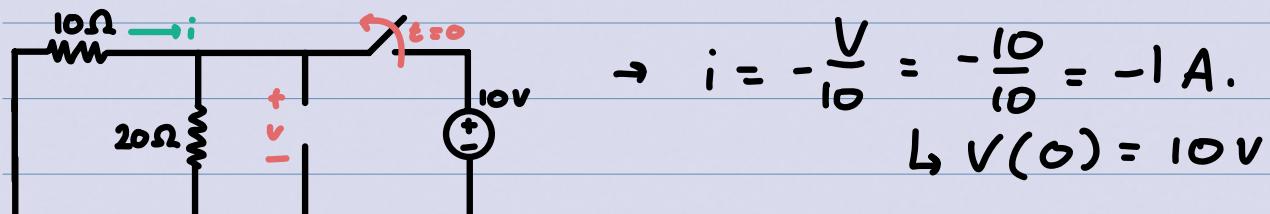for $t < 0$, $30u(t) = 0$ and the capacitor acts like an open switch:



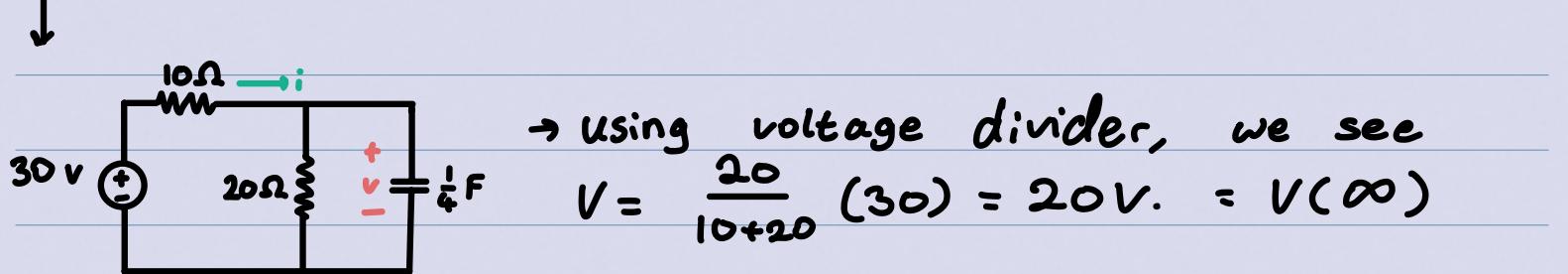for $t > 0$, $30u(t) = 30$ and the 10V source gets disconnected:



$$R_{Th} = 10 \parallel 20 = \frac{200}{30} = \frac{20}{3} \Omega.$$

↳ $\tau = R_{Th} C = \left(\frac{20}{3}\right) \left(\frac{1}{4}\right) = \frac{5}{3} s.$

$$\begin{aligned} V(t) &= V(\infty) + [V(0) - V(\infty)] e^{-t/\tau} \\ &= 20 + [10 - 20] e^{-\frac{3}{5}t} \rightarrow V(t) = 20 - 10e^{-0.6t} V \end{aligned}$$

$$i = \frac{v}{20} + C \frac{dv}{dt} = \frac{(20 - 10e^{-0.6t})}{20} + \frac{1}{4} (-0.6)(-10)e^{-0.6t} A$$

$$i = 1 - \frac{1}{2}e^{-0.6t} + \frac{3}{2}e^{-0.6t} = 1 + e^{-0.6t} A.$$


↳ $v = \begin{cases} 10 V, & t < 0 \\ (20 - 10e^{-0.6t}), & t \geq 0 \end{cases}$

$i = \begin{cases} -1 A, & t < 0 \\ 1 + e^{-0.6t} A, & t > 0 \end{cases}$

Step Response of an RL circuit:

↳ $i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$

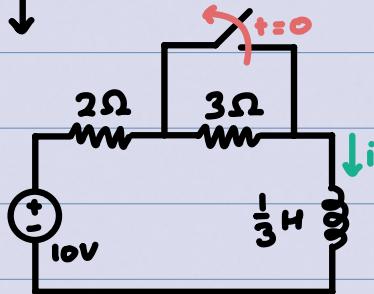Example: find $i(t)$ for $t > 0$. Assume that the switch has been closed for a long time.



when $t < 0$, the 3Ω resistor is short-circuited.
 $\therefore i(0) = 5A$.

when $t > 0$, the $R_{eq} = 5\Omega$. $\rightarrow \tau = \frac{L}{R} = \frac{1/3}{5} = \frac{1}{15} s$.

$$i(\infty) = \frac{V}{R_{eq}} = \frac{10}{5} = 2A.$$

$$i(t) = 2 + [5 - 2]e^{-t/1/15} = 2 + 3e^{-15t}$$

$$\hookrightarrow i(t) = \begin{cases} 5A, & t < 0 \\ 2 + 3e^{-15t}A, & t > 0 \end{cases}$$

Sinusoid : a signal that has the form of \sin / \cos

$$\hookrightarrow T = \frac{2\pi}{\omega}$$

$$\hookrightarrow A \cos(\omega t) + B \sin(\omega t) = C \cos(\omega t - \Theta)$$

where $C = \sqrt{A^2 + B^2}$, $\Theta = \tan^{-1} \frac{B}{A}$

phasors : complex numbers that represent the amplitude and phase of a sinusoid.

$$\cdot Z = x + yj = r \angle \phi = re^{j\phi} \quad \text{where } r = \sqrt{x^2 + y^2}, \phi = \tan^{-1} \frac{y}{x}$$

$$\therefore Z = x + yj = r \angle \phi = r (\cos \theta + j \sin \theta)$$

$$\text{multiplication: } Z_1 Z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

$$\text{division} : \frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \underline{\theta_1 - \theta_2}$$

$$\text{reciprocal} : \frac{1}{z} = \frac{1}{r} \angle \underline{-\theta}$$

$$\sqrt{\quad} : \sqrt{z} = \sqrt{r} \angle \underline{\theta/2}$$

$$\text{conjugate} : \bar{z} = r \angle \underline{-\theta} = x - yj = re^{-j\theta}$$

$$e^{\pm j\theta} = \cos\theta \pm j\sin\theta$$